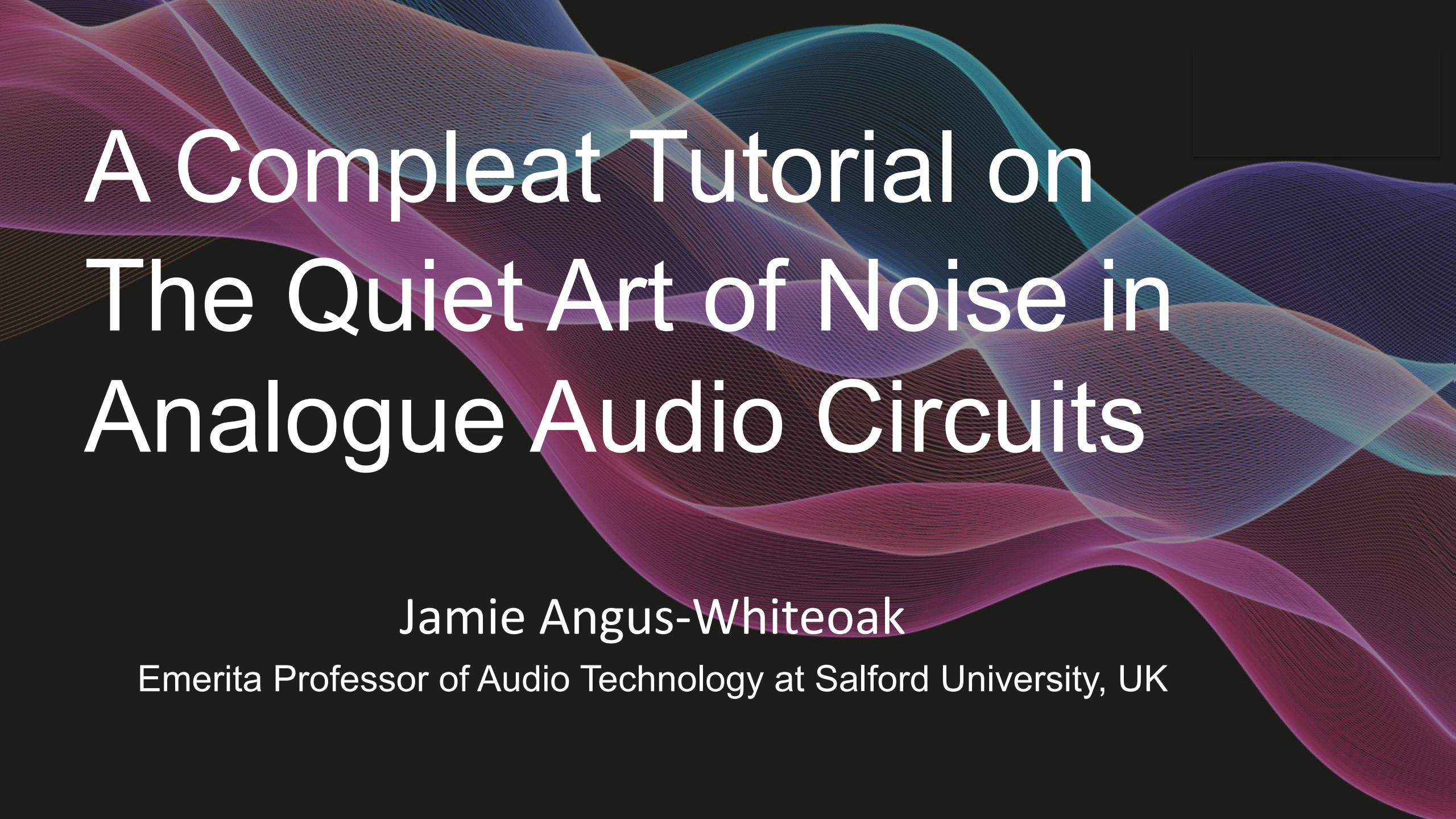




A Complete Tutorial on The Quiet Art of Noise in Analogue Audio Circuits

Jamie Angus-Whiteoak

Emerita Professor of Audio Technology at Salford University, UK




“The world may be digital...
But people are 4-wire and analogue!”

Jamie Angus-Whiteoak


Introduction

- Most of our audio processing happens in the digital domain
- However, there are still places in the audio chain that require low noise analogue circuits
- These are primarily at the beginning where transducers:
 - such as microphones
 - magnetic pick-up cartridges
 - tape heads, etc.
- Produce analogue signals that must be amplified prior to analogue to digital conversion
- low noise analogue circuits are also required at the digital to analogue convertors
 - Which often have challenging dynamic ranges

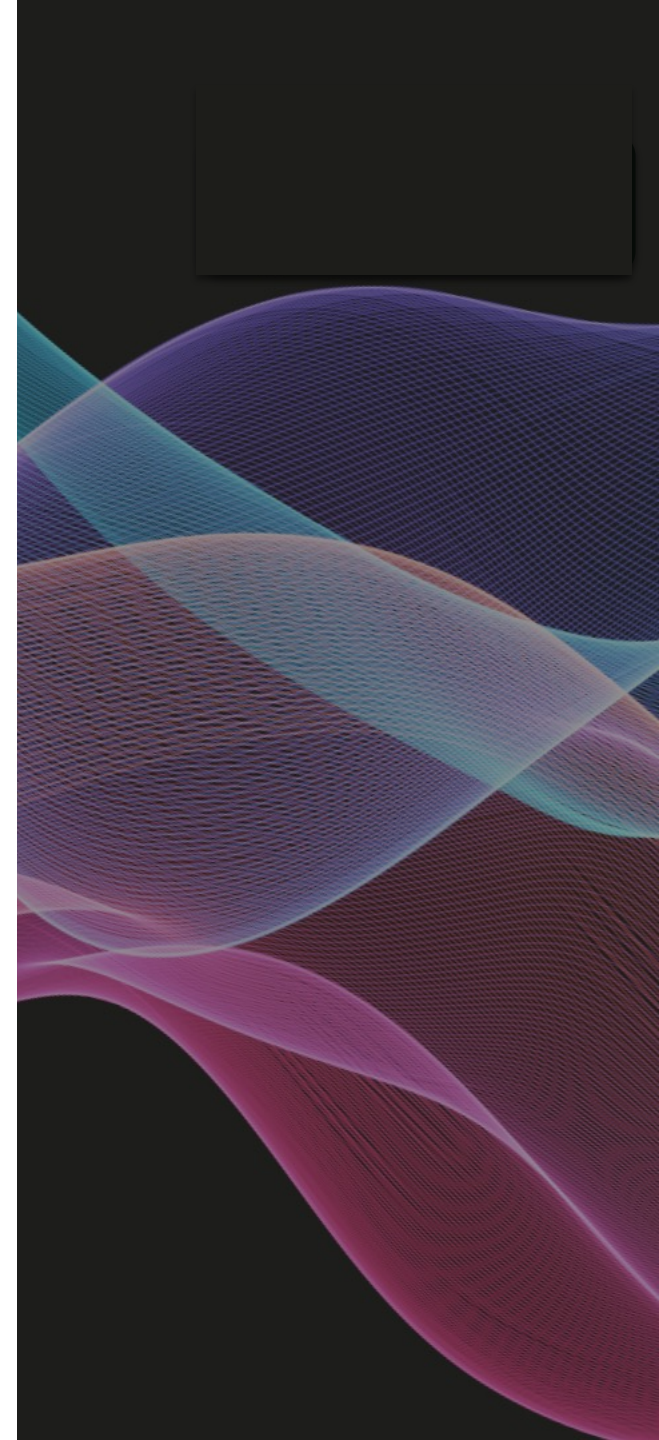


Introduction

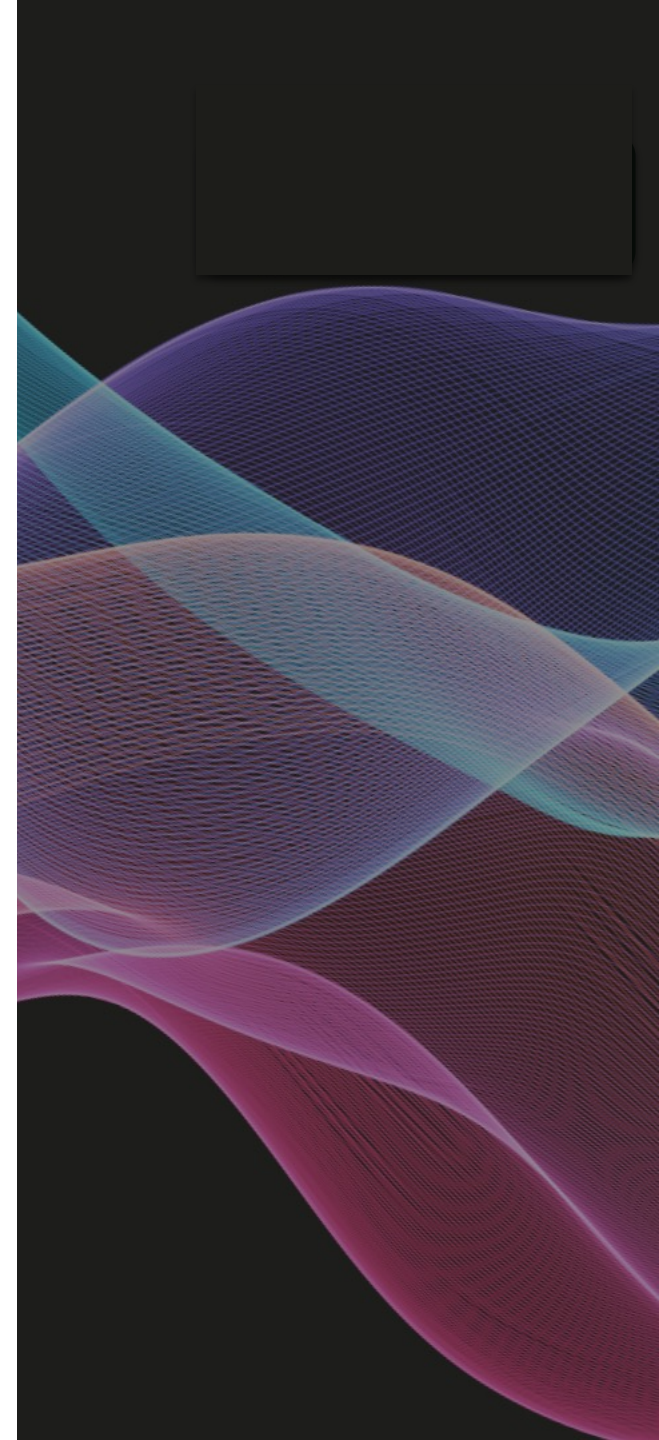- The purpose of this tutorial is to provide both an introduction to noise in audio circuits
- That takes account of reactive transducers
- And a framework for analysing noise
- And designing for it in:
 - Op-Amp
 - Transistor,
 - FET/MOSFET, and
 - Valve/tube circuits




Structure

- We will cover what sorts of noise occur in analogue circuits and devices.
- It will also develop a framework for identifying which components would work best in different situations and look at basic approaches to achieving low noise operation for a variety of transducers.
- It also will provide some "rules of thumb" for good practice for low noise circuit design.
- Then look at the application of the framework to a variety of electronic devices
- Finally, we will look at some speculative ideas for better low noise circuits.

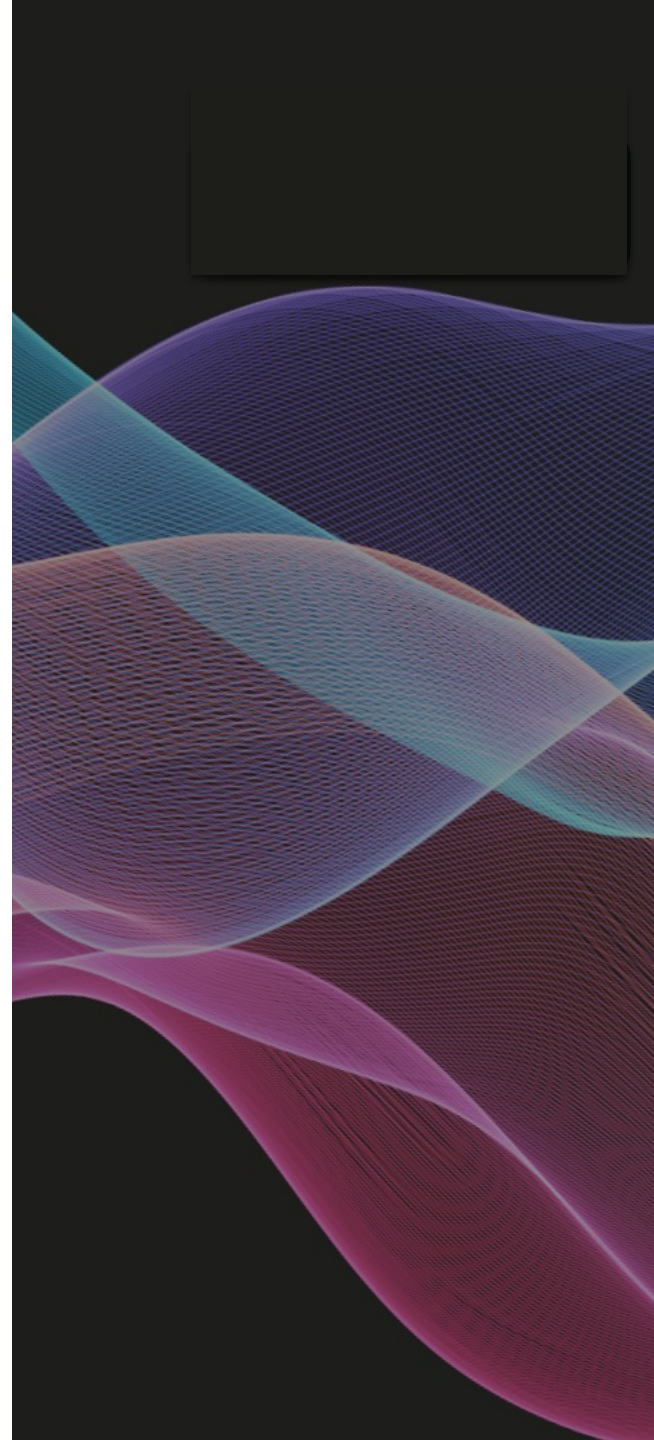

Thermal Noise


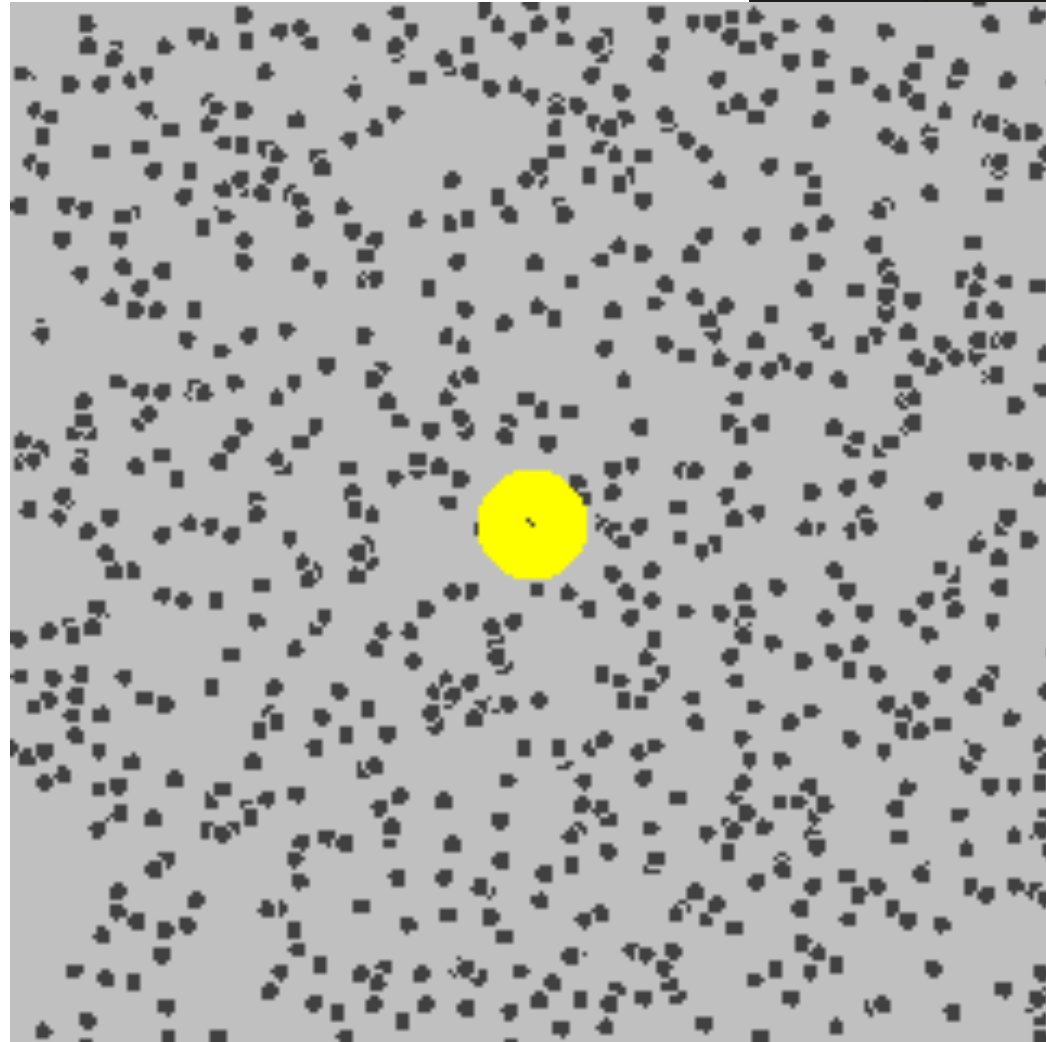
- Atoms and molecules vibrate above absolute zero
 - Due to thermal energy
 - Their vibration is random
- Brownian motion is evidence of this
- This means their electric fields vibrate as well
- And interact with any charge carriers in the material



<https://weelookang.blogspot.com/2010/06/ejs-open-source-brownian-motion-gas.html>

Thermal Noise

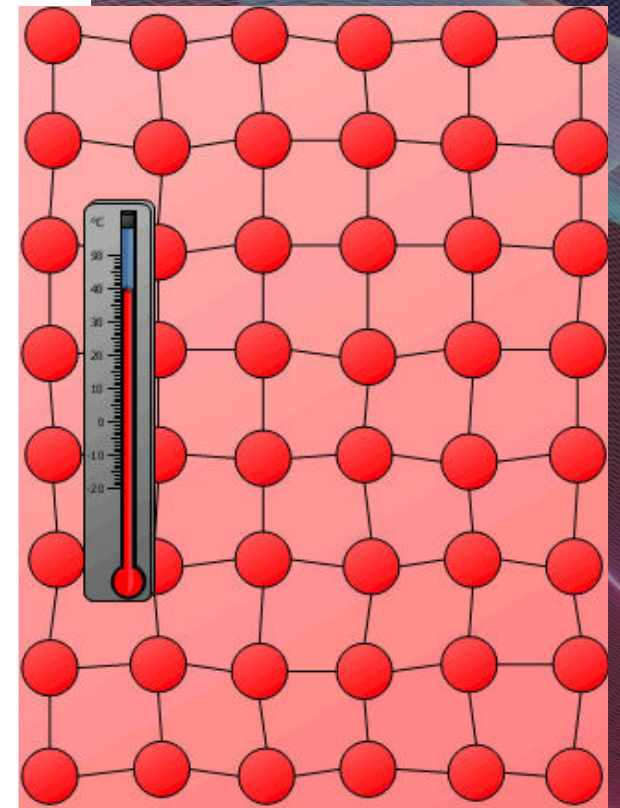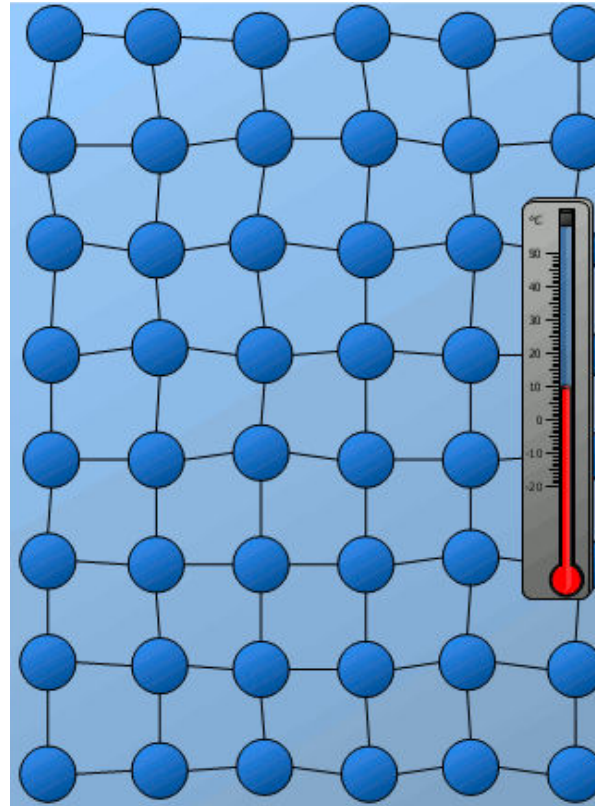
- Charge carriers (electrons and holes)
 - Interact with these vibrating electric fields
 - Generating voltage noise
- This Voltage noise is a function of both:
- Temperature
 - Higher temperatures mean more vibration
- And Resistance
 - There are more interactions (Collisions) with the material at higher resistances



<https://www.tec-science.com/thermodynamics/heat/heat-and-thermodynamic-equilibrium/>

Johnson-Nyquist Noise: Thermal Noise

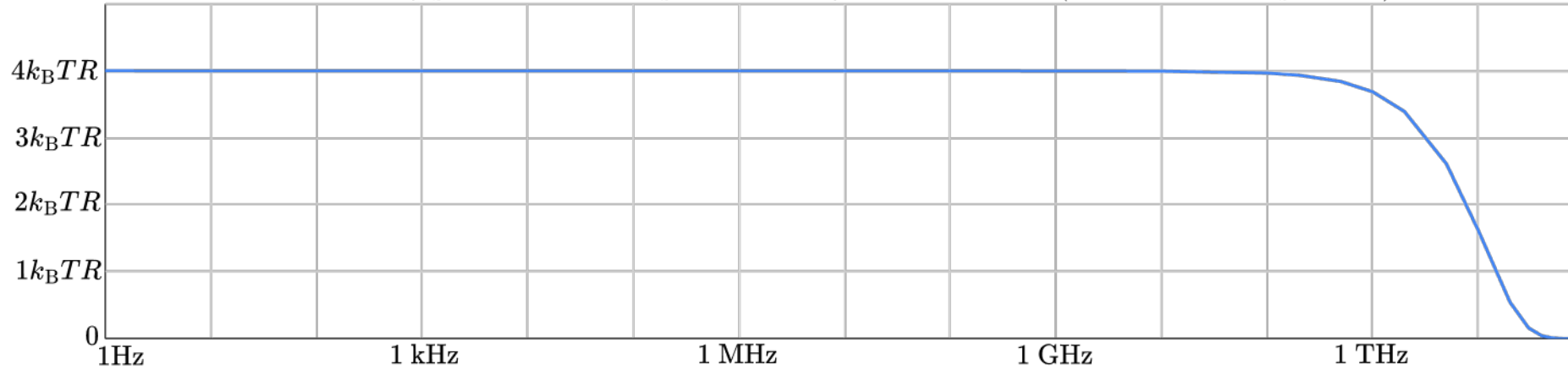
Johnson-Nyquist noise Power Spectral Density of Ideal Resistor (around room temperature)



- It is white noise. That is, flat within the audio band
- Any resistive component generates this type of noise
 - Including loss mechanisms in reactive transducers
- But reactive components like inductors or capacitors do not generate resistive noise
 - Like condenser/capacitive microphones
 - Magnetic pick ups and tape heads

Johnson-Nyquist Noise: Characteristics



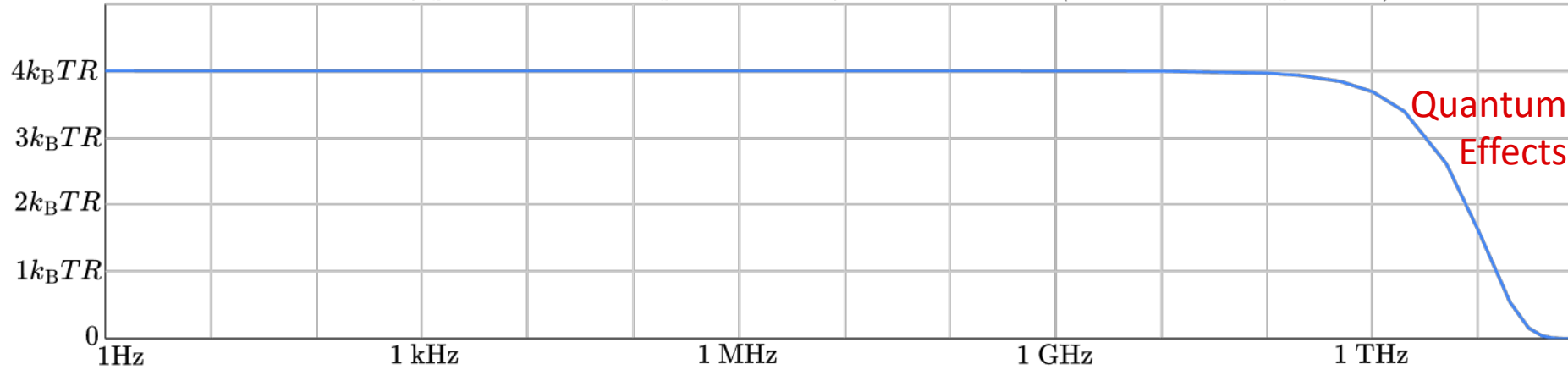
Johnson-Nyquist noise Power Spectral Density of Ideal Resistor (around room temperature)



- It is white i.e. flat within the audio band
- Its **Power** is proportional to:
 - Resistance (higher resistance means greater noise)
 - Temperature (higher absolute temperature means greater noise)
 - And Bandwidth (larger bandwidth means greater noise)
- Calculations must be done in the power domain
 - Or a proportional one like voltage squared or current squared


Johnson-Nyquist Noise: Modelling

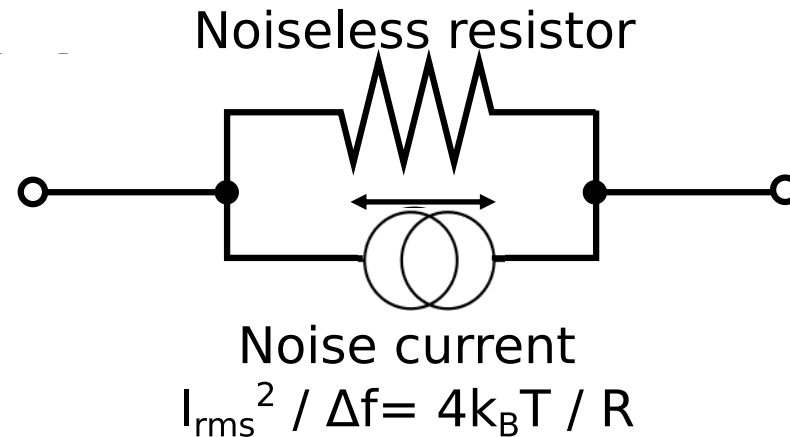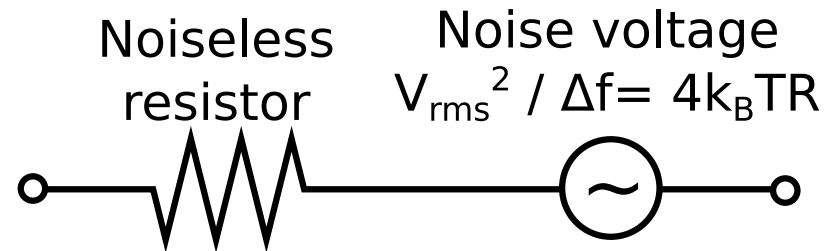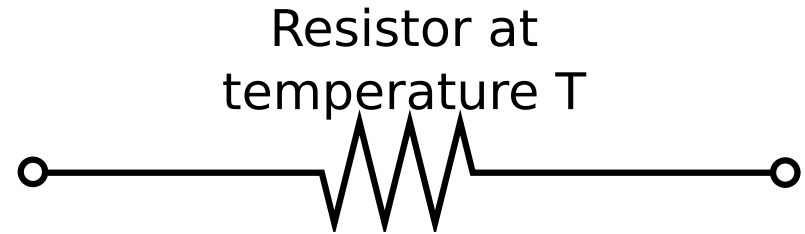- Can be modelled as a mean square noise voltage
 - In series with a noiseless resistor (R)
- Or be modelled as a mean square noise current
 - In parallel with a noiseless resistor (R)
- Δf is the Bandwidth (B)
- R is the Resistance in ohms
- K_B is Boltzmann's constant (1.380649×10^{-23} joules per kelvin)
- T is the absolute temperature (300K or 27°C for room temp)



Johnson-Nyquist Noise: Numbers

- The noise voltage V_n per $\sqrt{Hz}$ versus resistance is
 - $\sqrt{4k_B T} \sqrt{R} \approx 0.13 \sqrt{R} \text{ nV}/\sqrt{Hz}$
- Giving the following spectral voltage noise density values
 - $100\Omega \approx 1.3 \text{ nV}/\sqrt{Hz}$
 - $400\Omega \approx 2.6 \text{ nV}/\sqrt{Hz}$
 - $1k\Omega \approx 4.11 \text{ nV}/\sqrt{Hz}$
 - $10k\Omega \approx 13 \text{ nV}/\sqrt{Hz}$
- For the total noise multiply by the square root of the bandwidth, Δf , of 20kHz.
 - $\sqrt{20,000}$, which equals 141

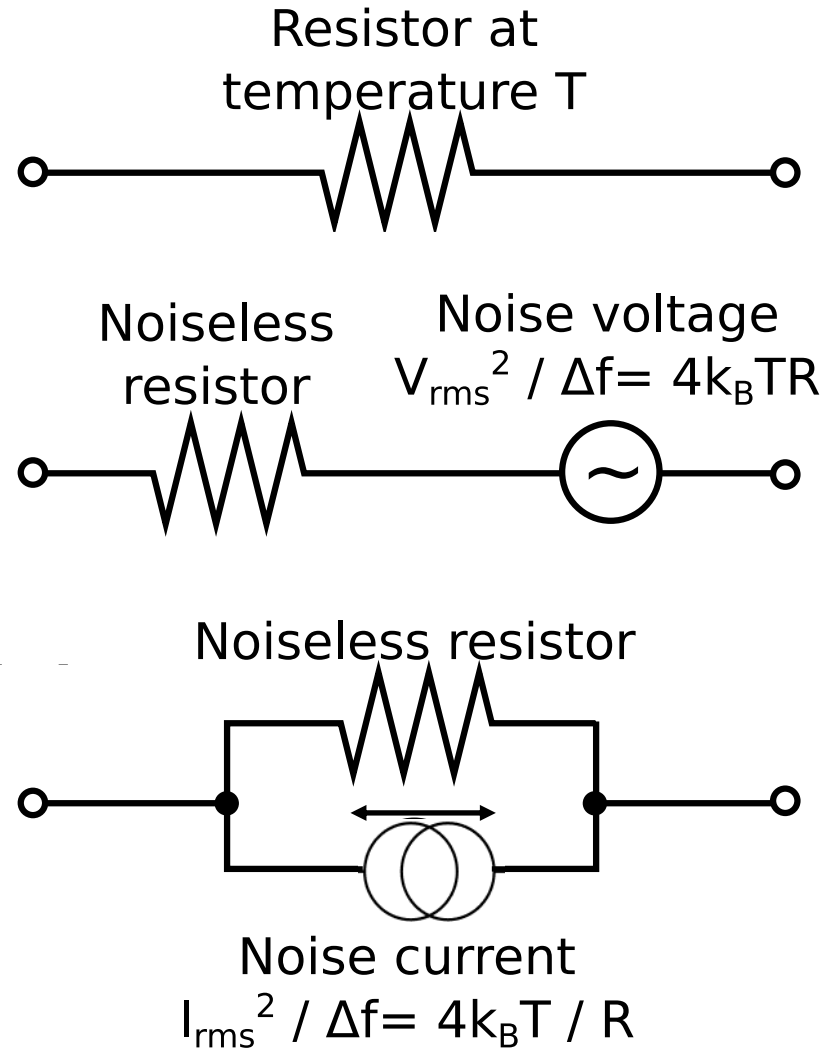

Shot (Current) Noise

- Charge carrier flow (current flow) is a random process
- Like rain...
- So, the current will have random fluctuations that is Current noise



<https://tenor.com/en-GB/view/rain-lights-park-tree-gif-15566169791114717094>

Shot Noise: Characteristics


- Need a point to measure shot noise such as:
 - A semiconductor junction
 - The grids in a valve/tube
- This results in Current Noise
 - That can generate noise across any impedance in a circuit
 - Including reactive impedances like inductors and capacitors
 - As well as resistors
- The noise is white
- And proportional to current flow
 - More current means more noise



https://25.media.tumblr.com/tumblr_m8bm7ukgJL1qhx5hjo1_400.gif

Shot Noise: Modelling

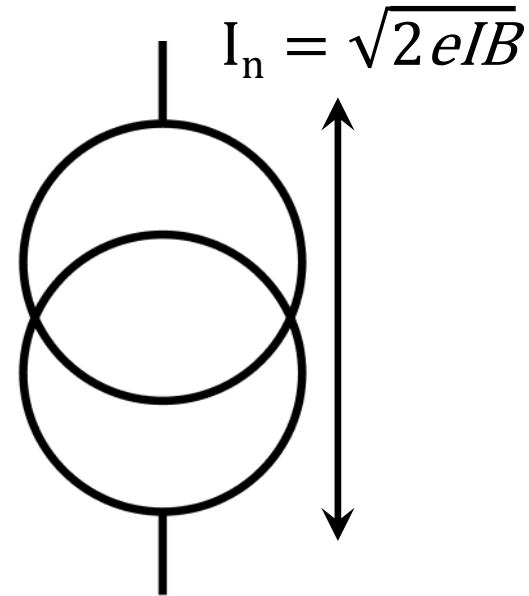- We can model shot noise as a current source
- With an rms noise of:
- $I_n = \sqrt{2eIB}$
Where:
 - I_n is the noise current in Amps
 - e is the charge on the electron (1.602×10^{-19} Coulombs)
 - I is the current in Amps
 - B is the Bandwidth (Δf) in Hz
- For the currents we use this can be quite small!




Shot Noise: Numbers

- The noise current I_n per $\sqrt{Hz}$ versus resistance is

$$I_n = \sqrt{2eI} \approx 0.57 \sqrt{I(\text{in } \mu A)} \text{ pA}/\sqrt{Hz}$$


- Giving the following spectral current noise density values

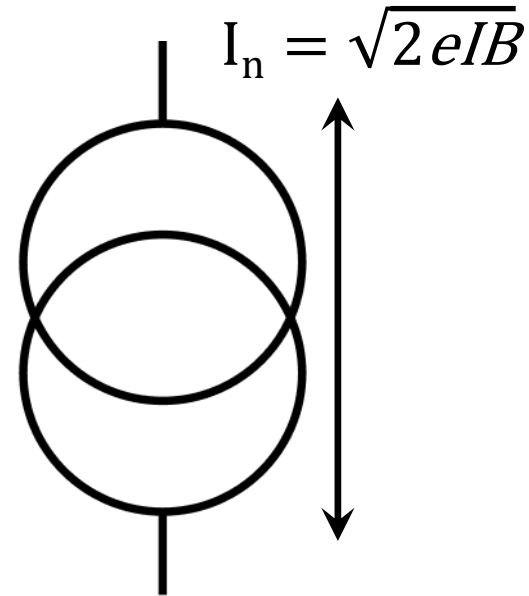- $1\mu A \approx 0.57 \text{ pA}/\sqrt{Hz}$
- $4\mu A \approx 1.14 \text{ pA}/\sqrt{Hz}$
- $10\mu A \approx 1.80 \text{ pA}/\sqrt{Hz}$
- $100\mu A \approx 5.7 \text{ pA}/\sqrt{Hz}$
- $1nA \approx 18.0 \text{ fA}/\sqrt{Hz}$
- $4mA \approx 36.0 \text{ pA}/\sqrt{Hz}$
- $10pA \approx 1.8 \text{ fA}/\sqrt{Hz}$





Partition Noise

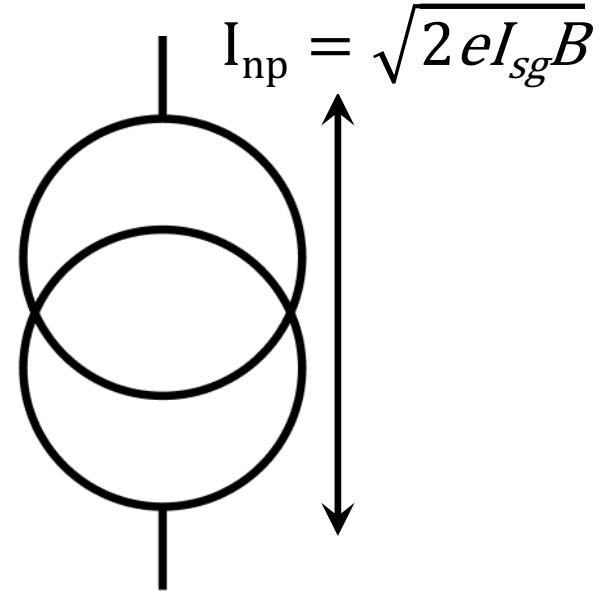- Partition noise is another name for shot noise
- It happens when current is split into two streams
- Usually used in tubes/valves to account for the excess noise contributed by extra grids in the system
- Can be derived from the same equations as shot noise
- $I_{np} = \sqrt{2eI_{sg}B}$





Excess, Flicker, or 1/f Noise

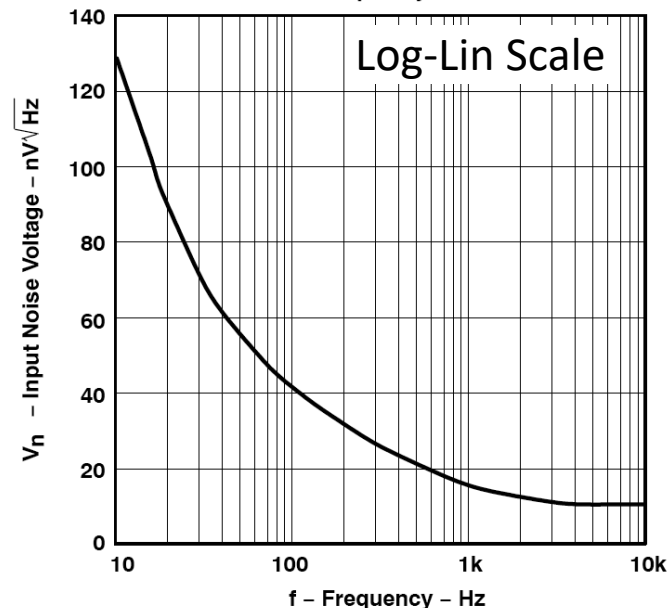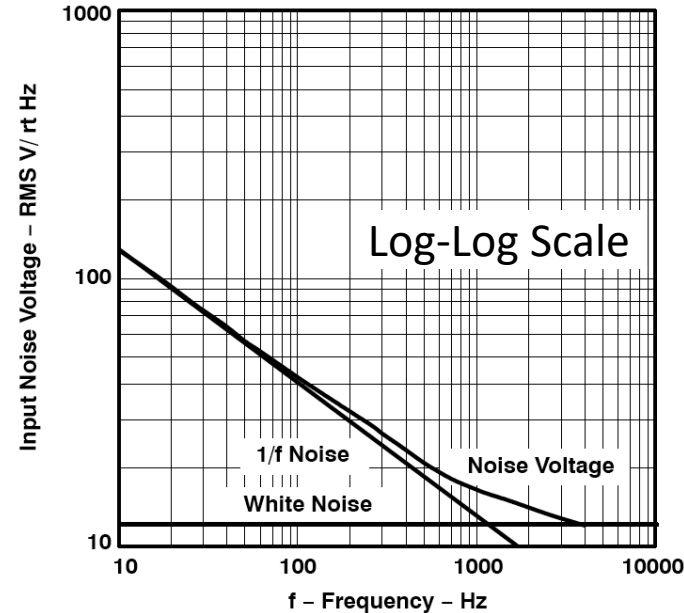- It is in excess of the usual thermal or shot noise
- It has a $1/f$ power spectral density.
- It is therefore often referred to as $1/f$ noise or pink noise
- It occurs in almost all electronic devices
- Due to a variety of effects,
 - Such as impurities in a conductive channel,
 - Generation and recombination noise in a transistor
 - Surface states in a MOSFET
 - Cathode emission variation




Excess, Flicker, or 1/f Noise

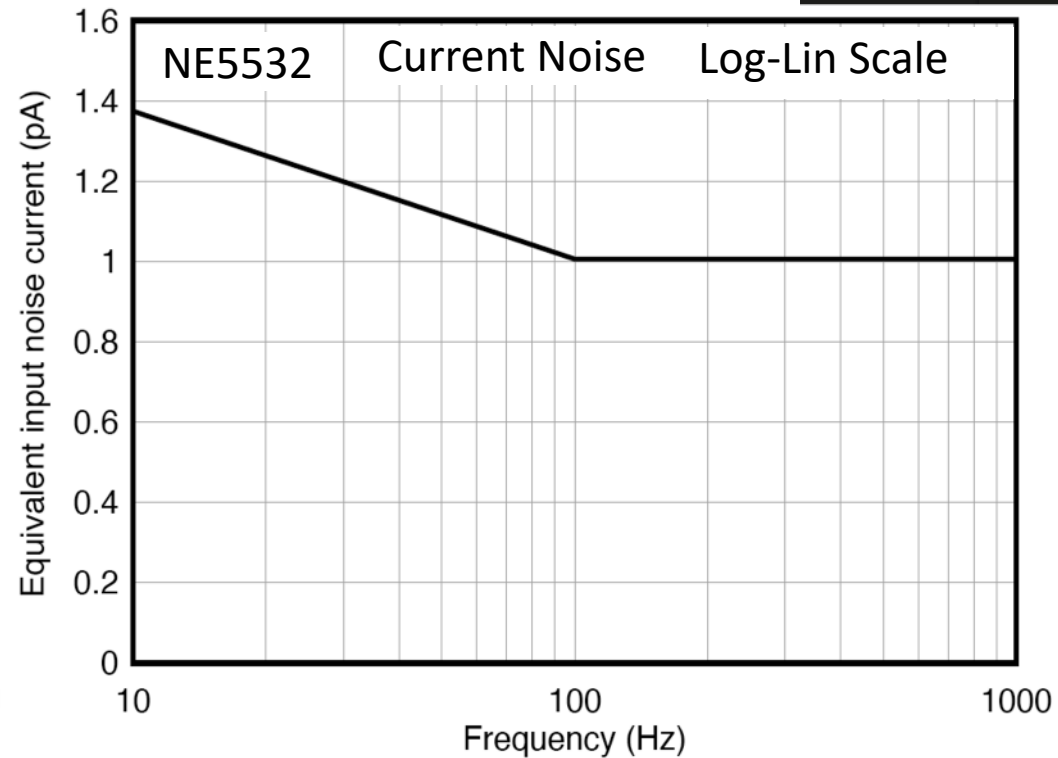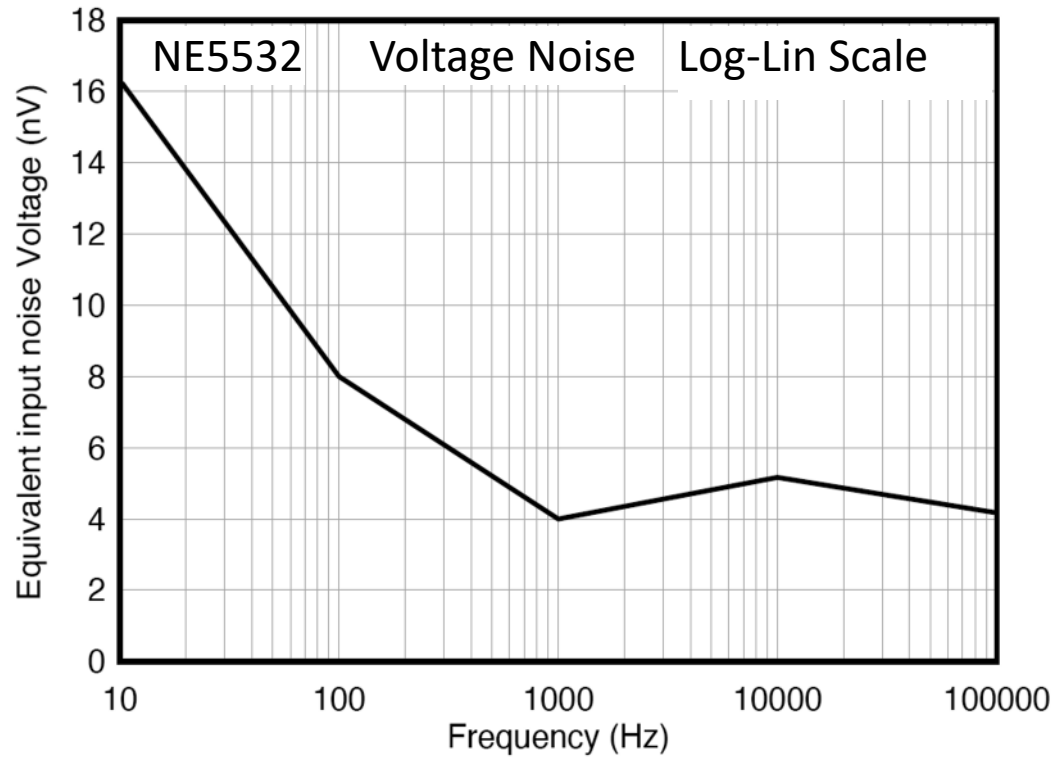


- 1/f noise can happen in both
 - The voltage noise
 - And the current noise
- For example, the NE5532
- Can also have “popcorn” noise which increases at $> 1/f^2$

Simple Amplifier Noise Model

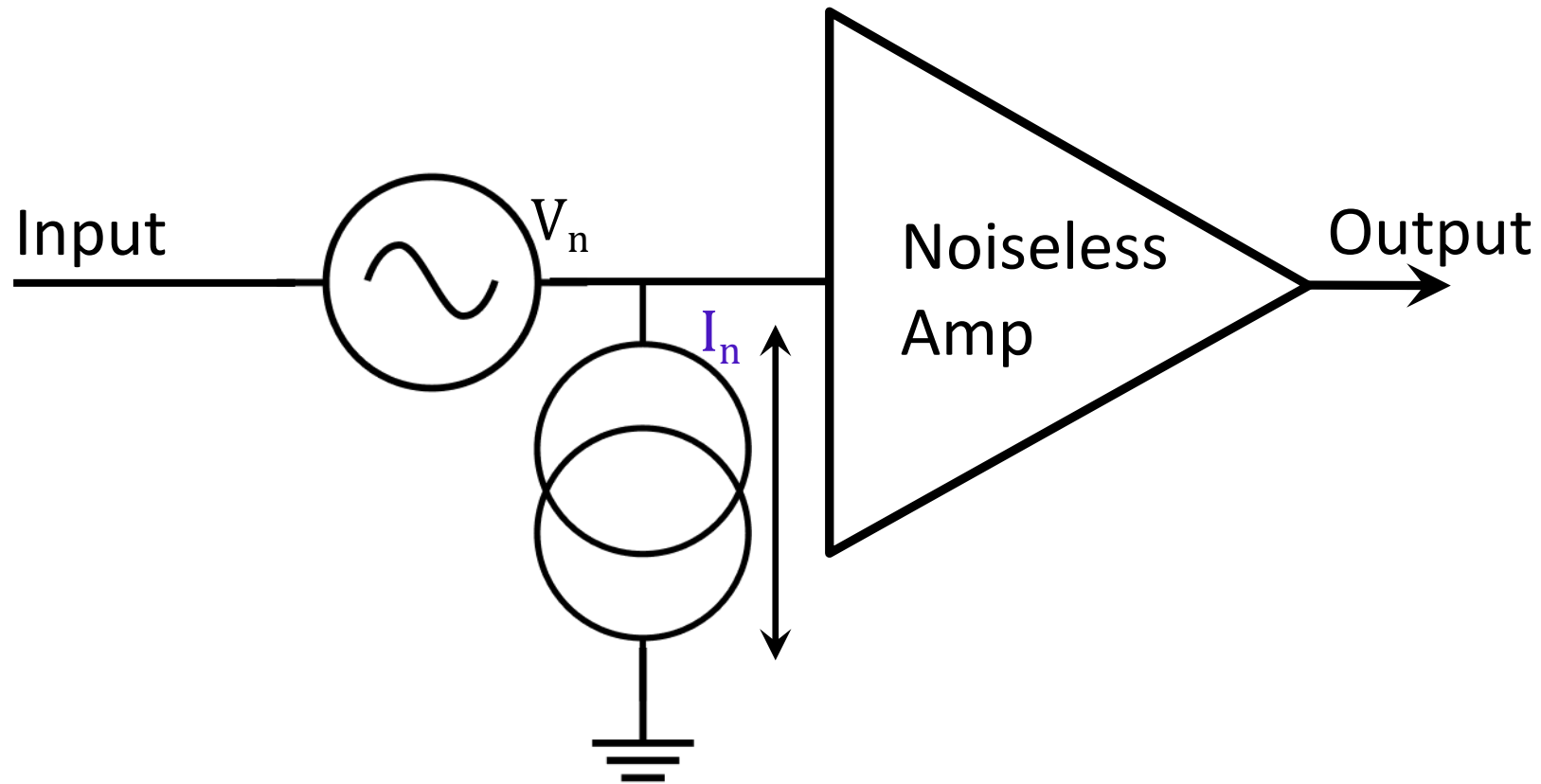


- Has two noise sources:
 - Voltage noise V_n
 - Current noise I_n
- Applicable to all devices

Amplifier Noise Model: Resistive Source

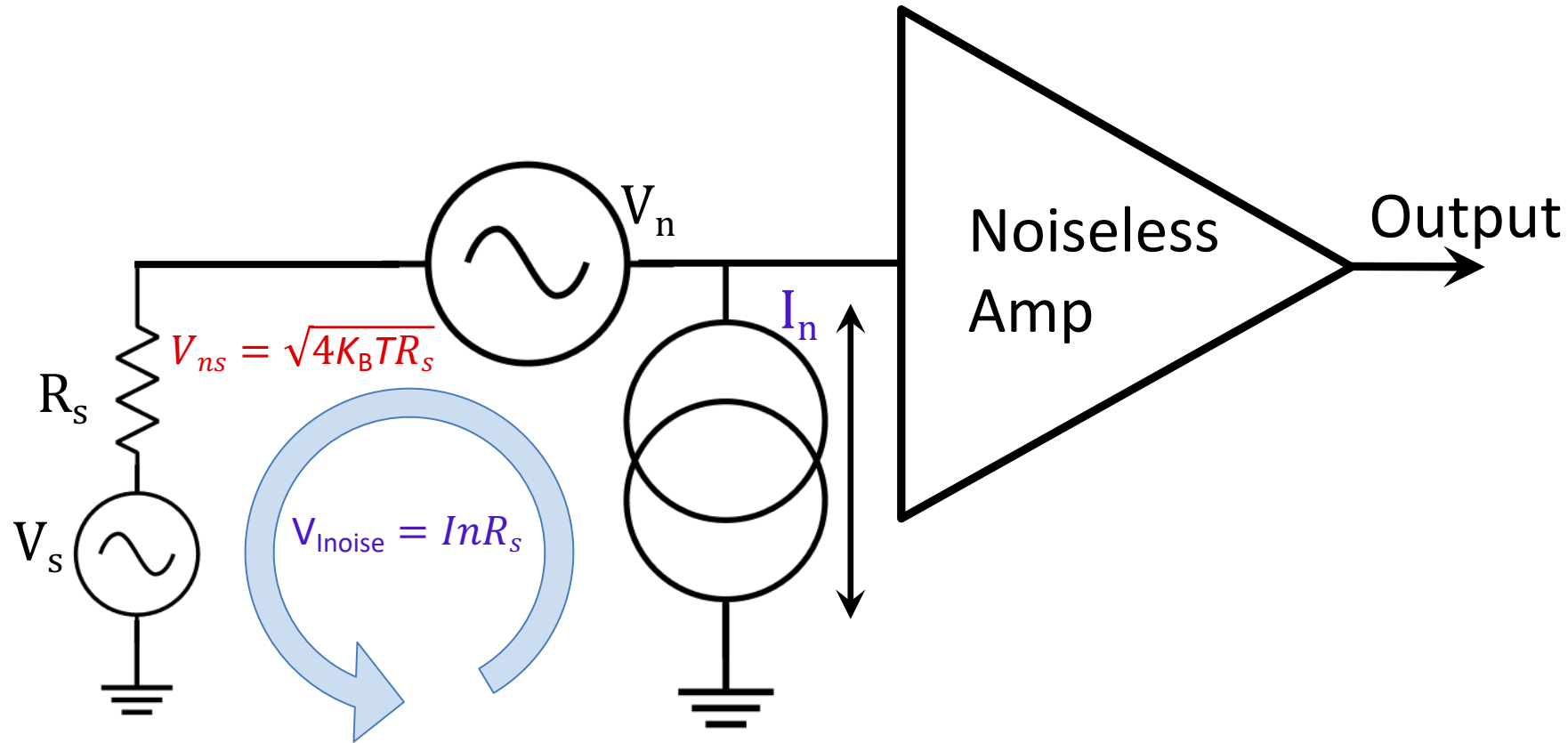

- Resistance of the source will generate a voltage noise (V_{ns})
 - Which will add to the amplifier's noise voltage (V_n)
- It will also generate an additional noise voltage (V_{Inoise})
 - Due to the amplifier's noise current flowing through it.

Amplifier Noise Model: Resistive Source

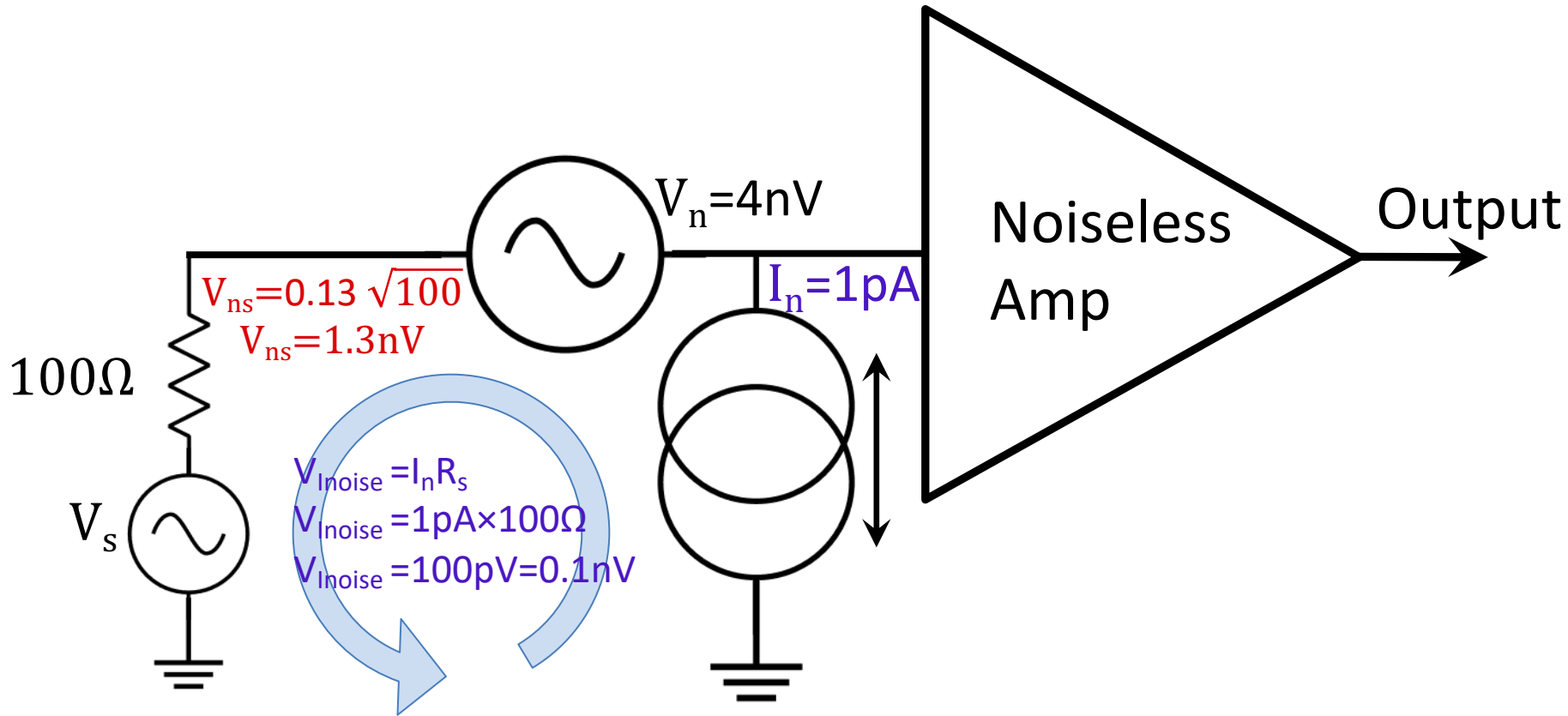


- Add the squared noises to get the total noise V_{total} (All per $\sqrt{\text{Hz}}$)
 - $V_{\text{total}} = \sqrt{V_{ns}^2 + V_n^2 + V_{Inoise}^2}$
 - For $R_s = 100\Omega$, and an NE5532 ($V_n = 4\text{nV}/\sqrt{\text{Hz}}$, $I_n = 1\text{pA}/\sqrt{\text{Hz}}$)
 - $V_{\text{total}} = \sqrt{(1.3\text{nV})^2 + (4\text{nV})^2 + (0.1\text{nV})^2} = 4.21\text{nV}/\sqrt{\text{Hz}}$! (10.21dB noise figure)



Side Bar: The Effect of Squared Adding

A	B	B	Result	(Result/A) in dB
1	1.000	$1/1$	1.414	3.010
1	0.500	$1/2$	1.118	0.969
1	0.316	$1/\sqrt{10}$	1.049	0.414
1	0.250	$1/4$	1.031	0.263
1	0.100	$1/10$	1.005	0.043

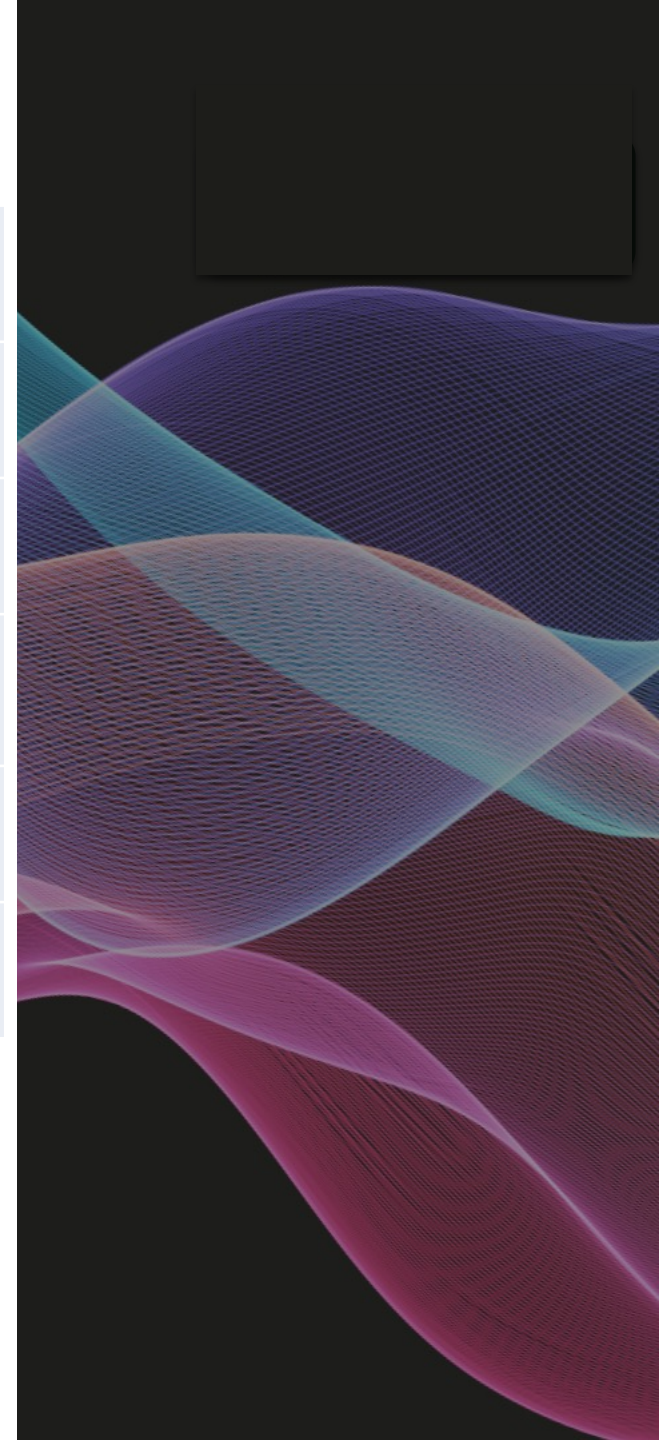
- As the numbers become different
 - Then the smaller one of the two rapidly disappears!
- Once they are a factor of 10 different
 - The smaller one becomes irrelevant



Transformers

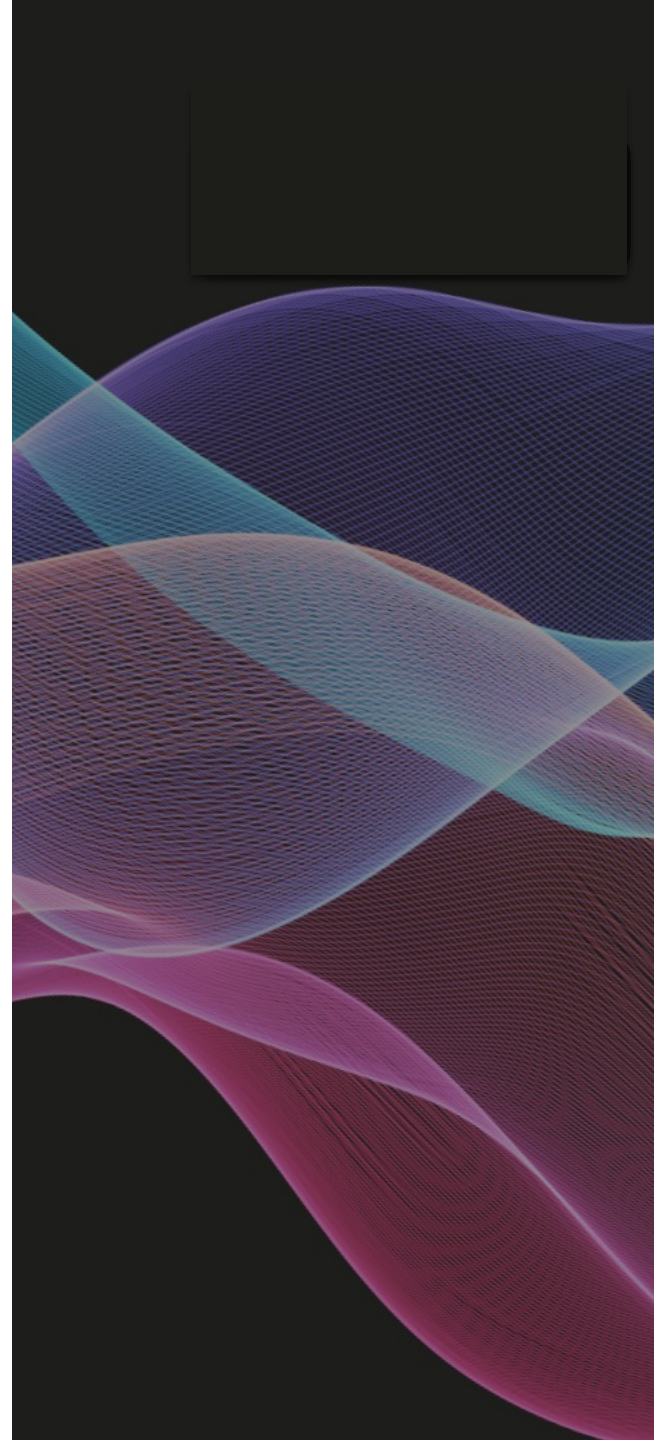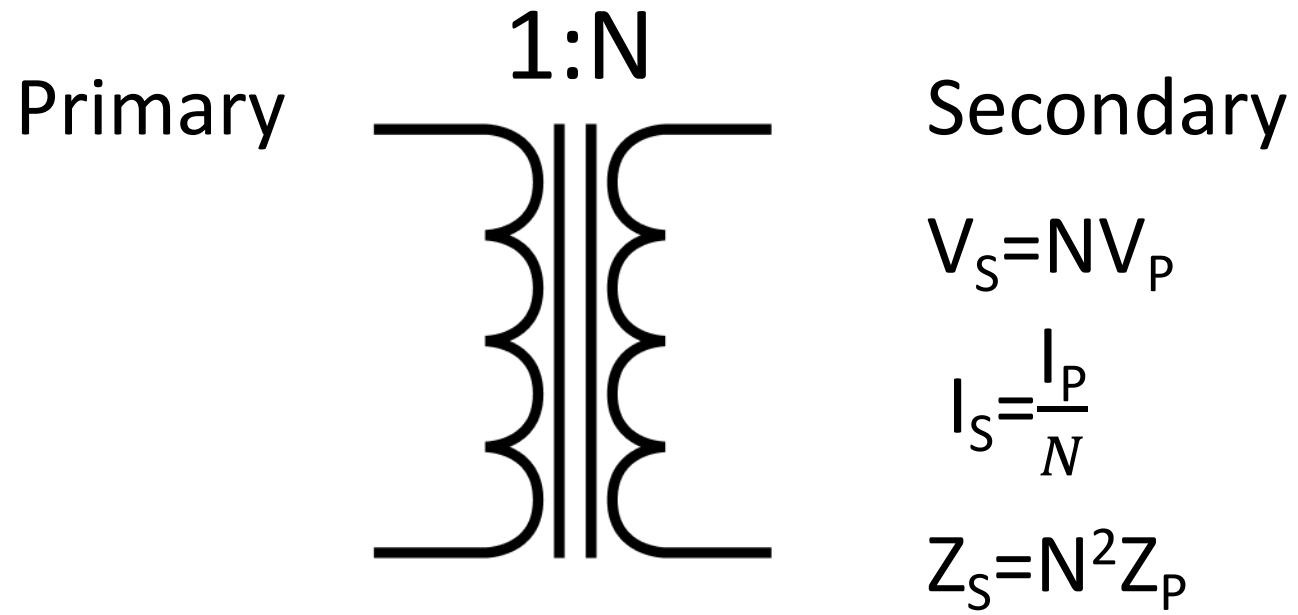


How Can We Do Better? Use a Transformer

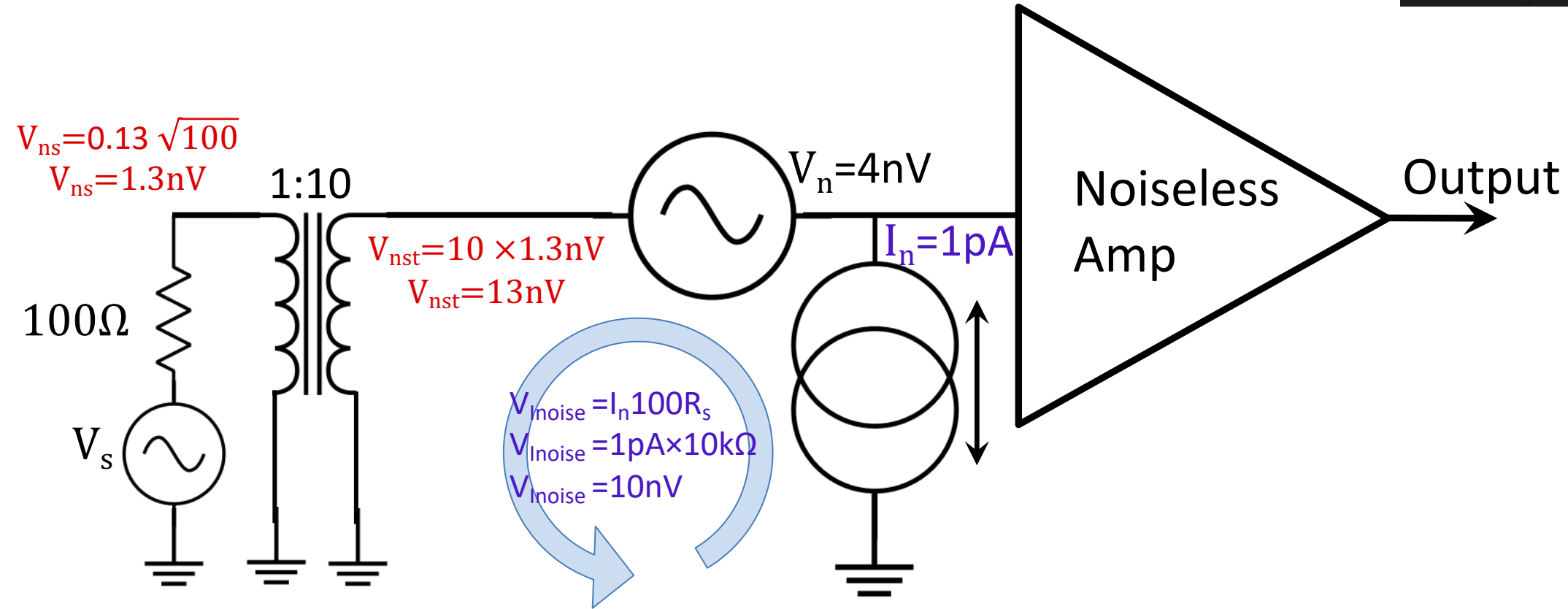


- Add the squared noises to get the total noise V_{total} (All per $\sqrt{\text{Hz}}$)
 - $V_{\text{total}} = \sqrt{V_{nst}^2 + V_n^2 + V_{\text{noise}}^2}$
 - For $R_s = 100 \Omega$, and an NE5532 ($V_n = 4 \text{ nV}/\sqrt{\text{Hz}}$, $I_n = 1 \text{ pA}/\sqrt{\text{Hz}}$)
 - $V_{\text{total}} = \sqrt{(13 \text{ nV})^2 + (4 \text{ nV})^2 + (10 \text{ nV})^2} = 16.9 \text{ nV}/\sqrt{\text{Hz}}$! (2.28dB noise figure)

Is There An Optimum Source Resistance

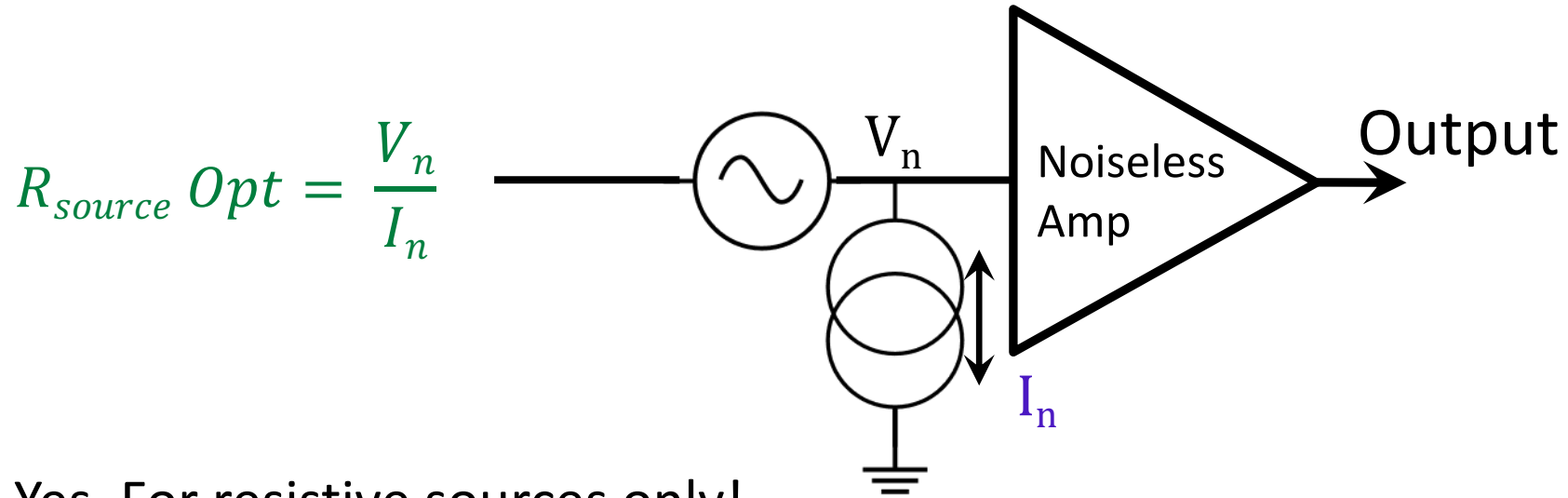


- Yes, For resistive sources only!
- You get the lowest noise figure if the source resistance is equal to:
 - The amplifier's voltage noise V_n
 - Divided by its current noise I_n
- This results in the noise voltage
 - Due to the noise current flowing in the source
 - Being equal to the amplifier's voltage noise
- It can be achieved by choosing an appropriate turns ratio for the transformer.

Is There An Optimum Transformer Ratio

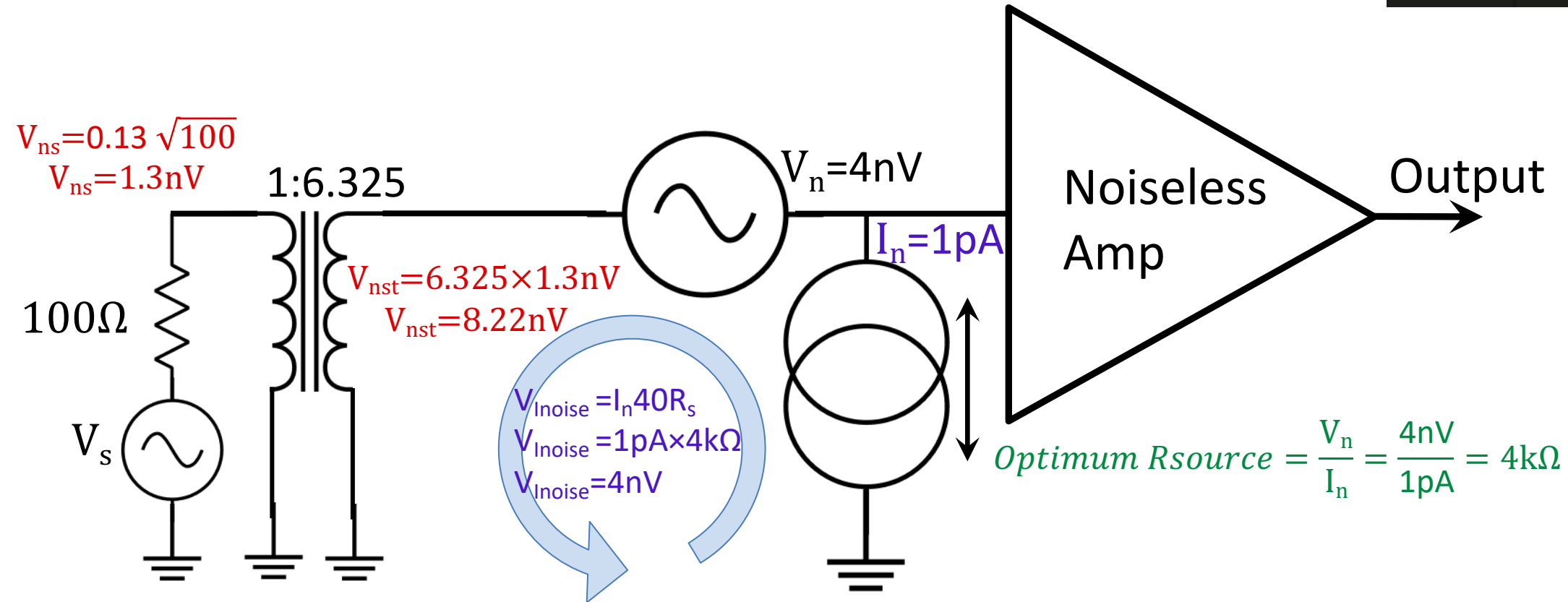


- Add the squared noises to get the total noise V_{total} (All per $\sqrt{Hz}$)
 - $V_{total} = \sqrt{V_{nst}^2 + V_n^2 + V_{Inoise}^2}$
 - For $R_s = 100\Omega$, and an NE5532 ($V_n = 4\text{nV}/\sqrt{Hz}$, $I_n = 1\text{pA}/\sqrt{Hz}$)
 - $V_{total} = \sqrt{(8.22\text{nV})^2 + (4\text{nV})^2 + (4\text{nV})^2} = 16.9\text{nV}/\sqrt{Hz}$! (1.68dB noise figure)

Amplifier Noise Model: Inductive Source

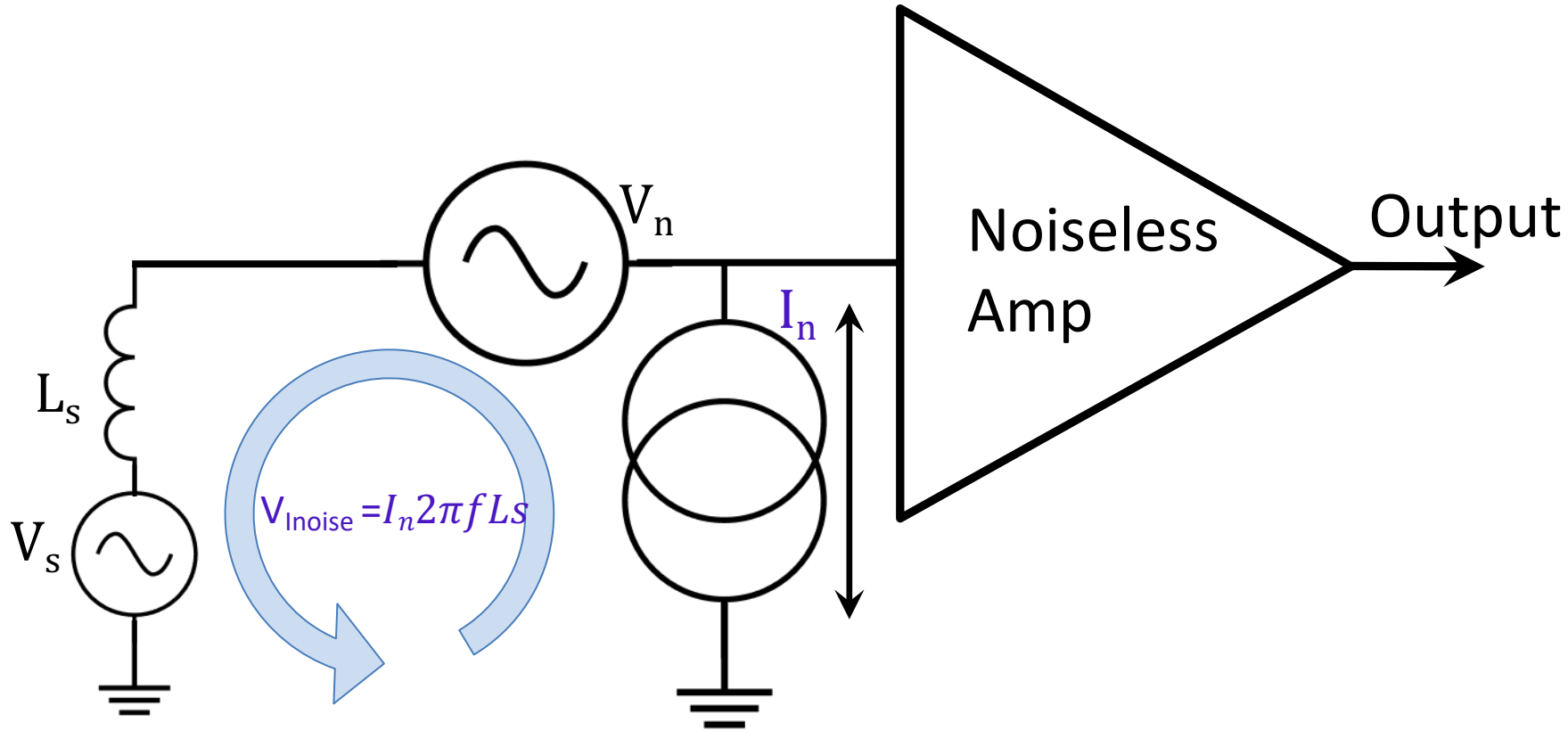


- For an inductive source like a magnetic playback head or phono cartridge
- The noise induced by the current noise rises with frequency
- There is no optimum source impedance
- One needs low current noise and low voltage noise
- As the series resistance may also be quite low

Amplifier Noise Model: Capacitive Source

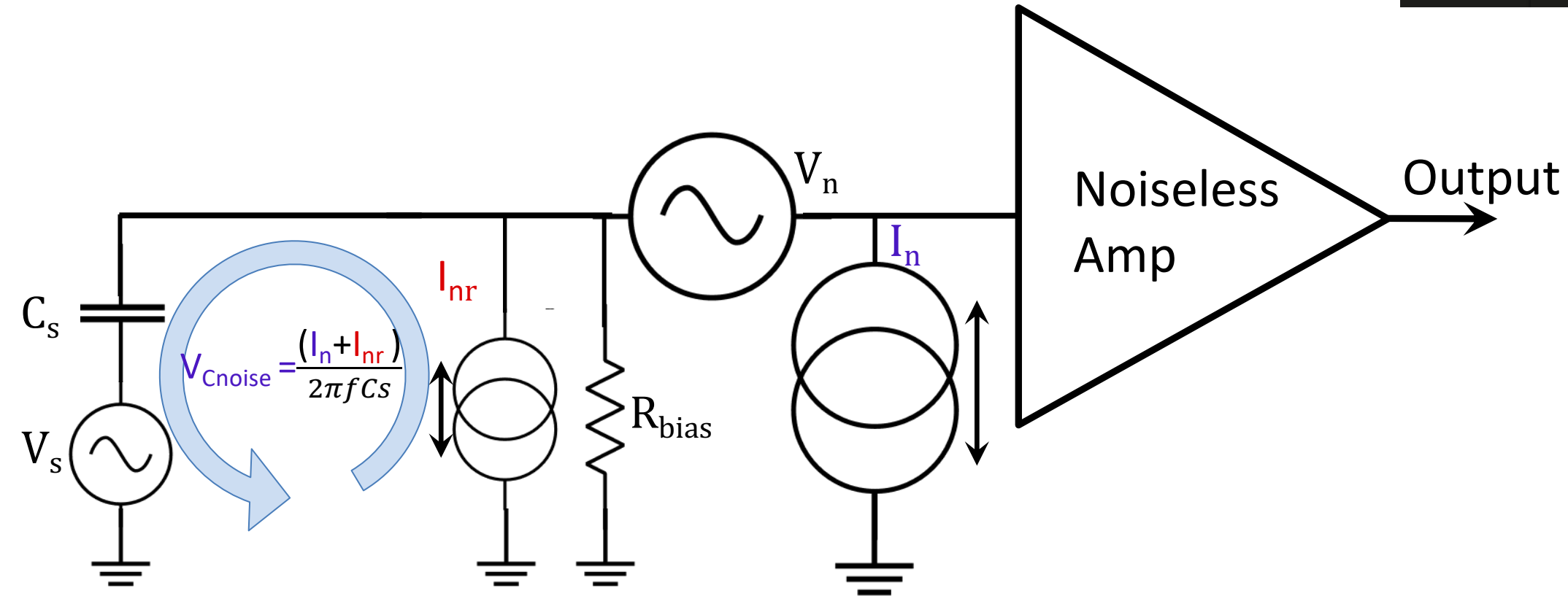


- For capacitive sensor's, the impedance is highest at low frequencies (30pF = 265M Ω at 20Hz)
- And the noise falls with frequency
- So, I_n needs to be low
- But the dominant source of noise is R_{bias} which needs to be as high as possible

Does Every Stage Have to Have Low Noise?

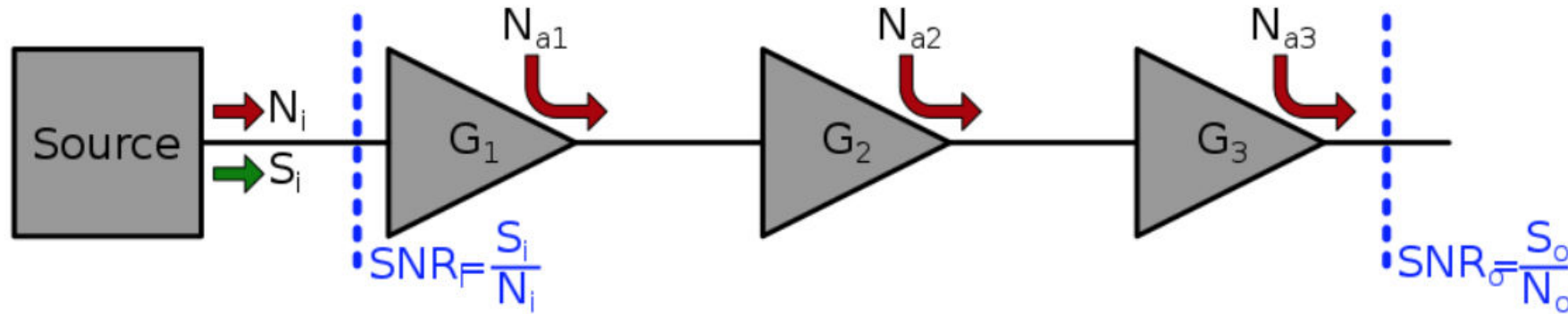


- The first stage in the system dominates the noise
 - Providing the first stage gain is high enough
 - A gain of 10 is usually enough
- The first stage increases the size of the signal thus reducing the effect of the noise in the second stage
 - Unless the second stage noise is outrageous!

Inverting Amplifier Noise

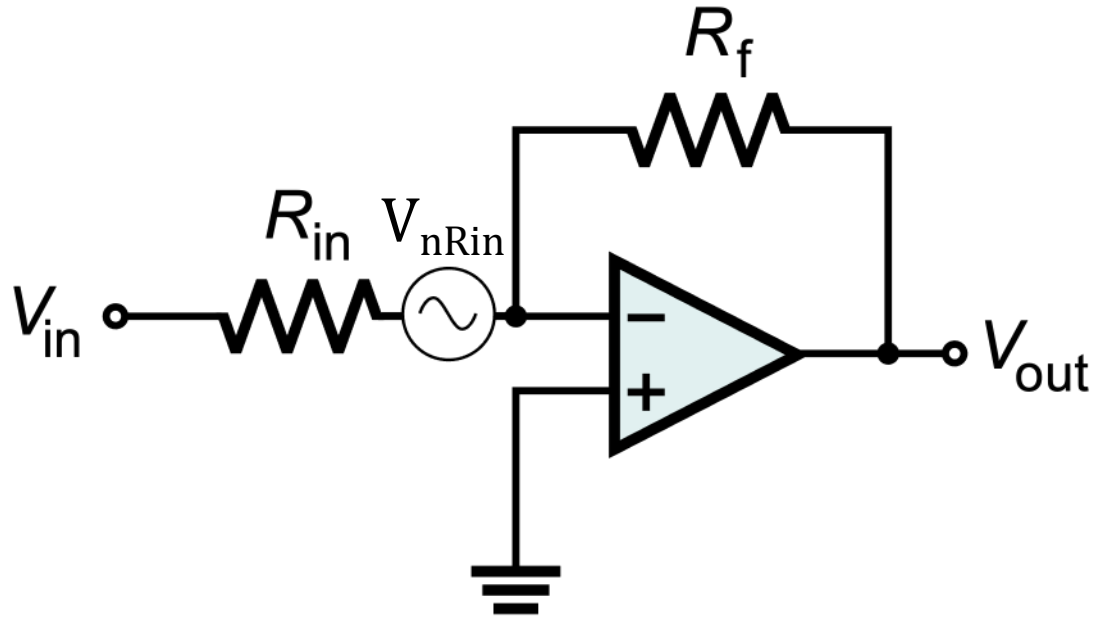



- An inverting amplifier puts a resistor in series with the input
- This is a very bad idea as it means you have put an additional voltage noise source between your source and the amplifier
- Do not do this:
 - Unless the transducer is effectively R_{in}
 - Or R_{in} is very small!

Non-Inverting Amplifier Noise

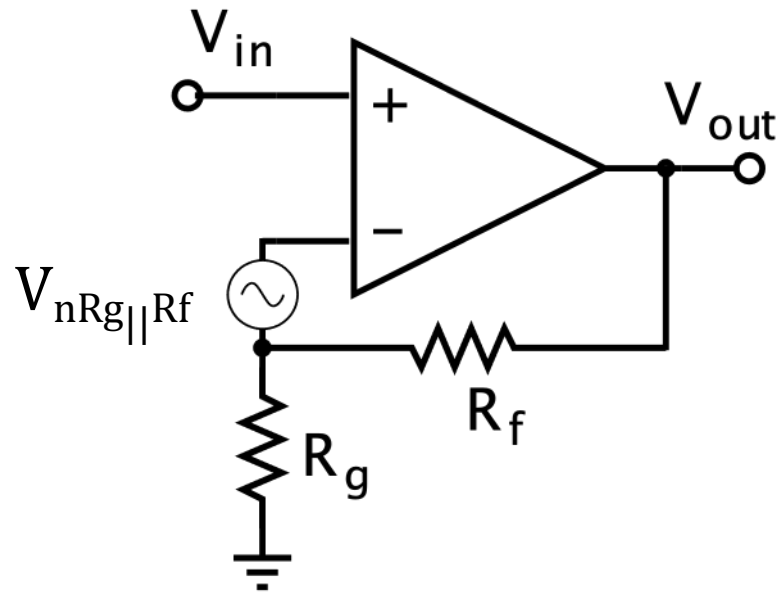

- A non-inverting amplifier avoids putting a resistor in series with the input
- However, you must ensure that the parallel combination of R_g and R_f
 - Are small enough so that they generate less noise voltage than V_n
- Also, the necessary bias resistor on the +input should be significantly larger than the source impedance to avoid noise


Summing Amplifier Noise: Hidden Gain

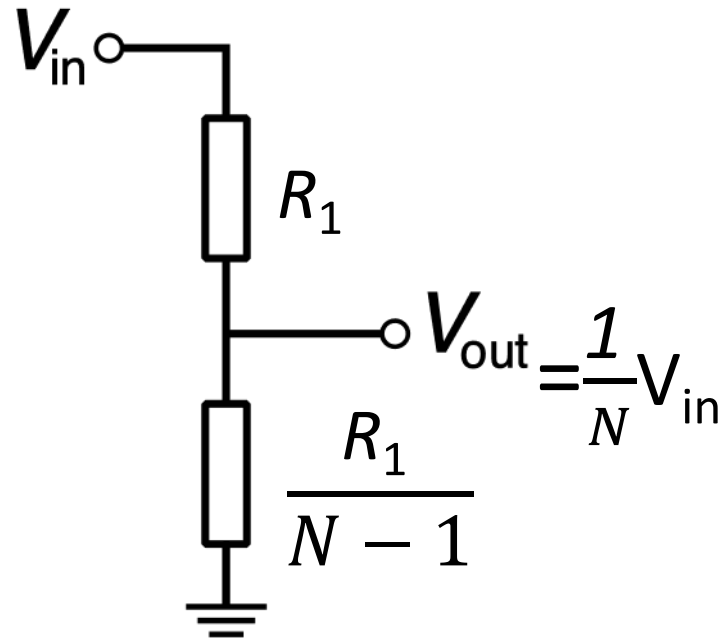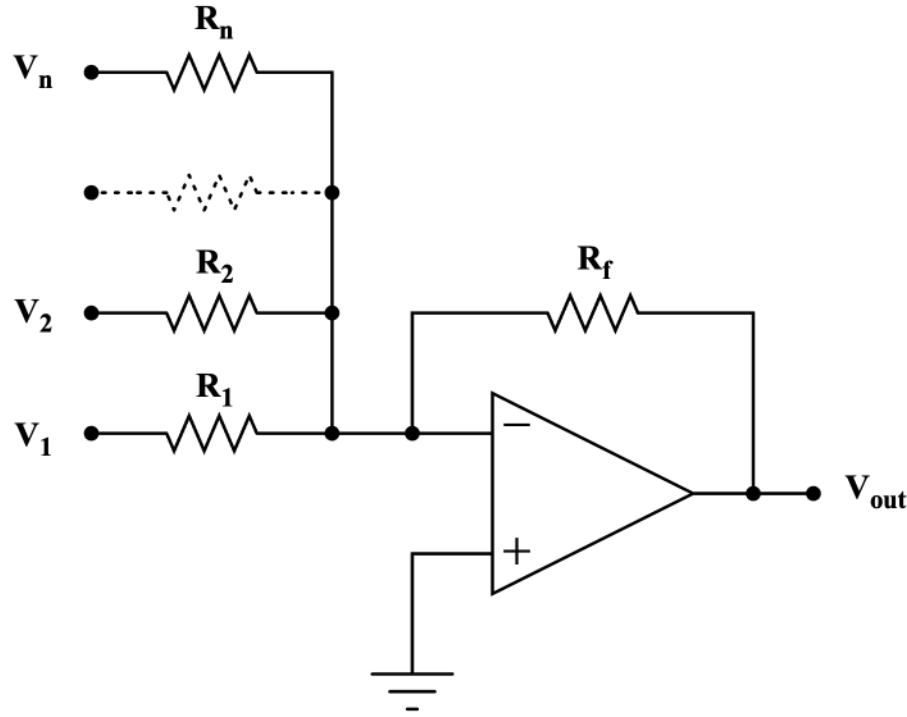



- A summing amplifier effectively attenuates the signal and then reamplifies it
- The other inputs act in parallel to form an attenuator
 - But there is a compensating attenuation in the feedback path
 - So, the end-to-end gain is one, but the internal gain can be high!
- Also, happens in equalisers and high Q filters

Equaliser Amplifier Noise: Hidden Gain

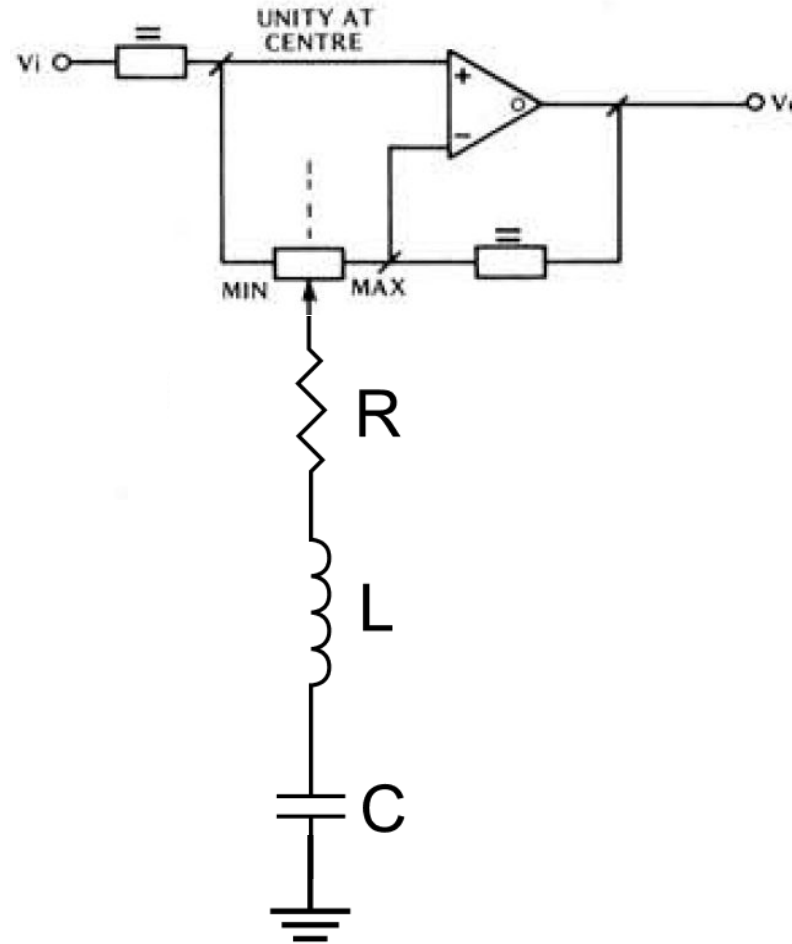- A summing amplifier effectively attenuates the signal and then reamplifies it
- The other inputs act in parallel to form an attenuator
 - But there is a compensating attenuation in the feedback path
 - So, the end-to-end gain is one, but the internal gain can be high!
- Also, happens in equalisers and high Q filters




Noise in Bipolar Transistors

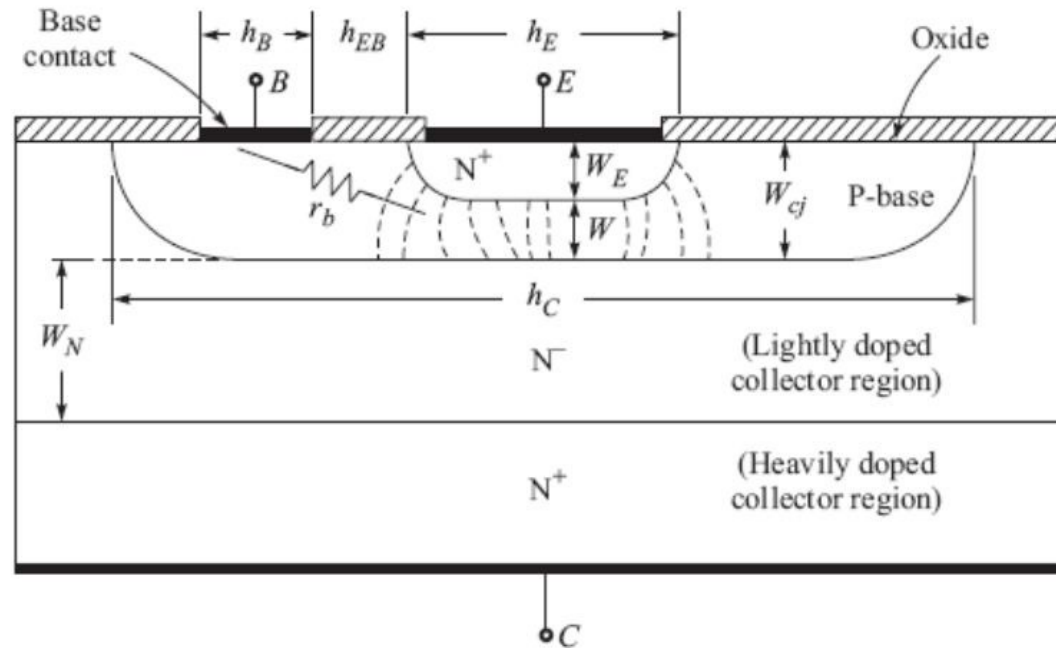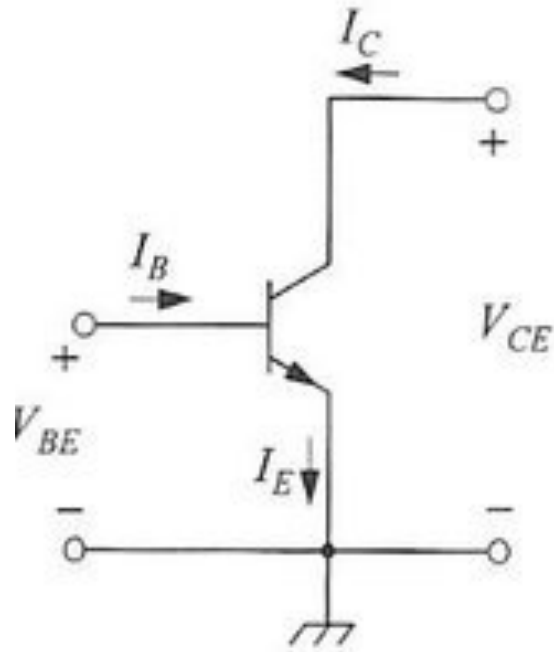



- The voltage noise (V_n) depends the collector current which defines the transconductance $gm = 40I_C$
 - The noise resistance is $R_{noise} = \frac{1}{gm} + r_{bb'} = \frac{25}{I_C} + r_{bb'}$ (I_C in mA)
 - As current increases noise goes down but limited by $r_{bb'}$
- The current noise (I_n) depends on the base current
 - Which is related to the collector current by the current gain

1/f Noise in Bipolar Transistors

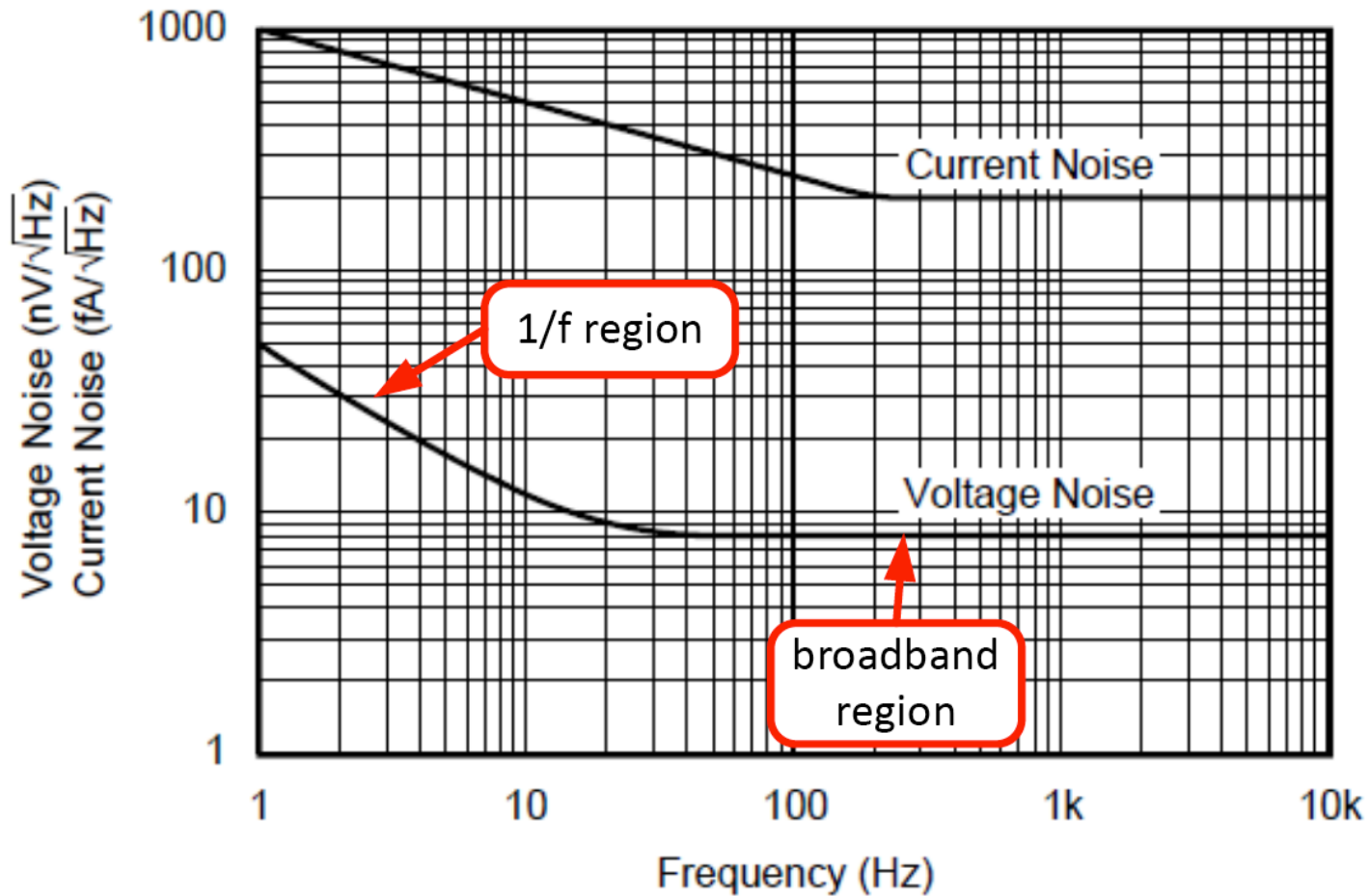



- There is 1/f noise in both current and voltage noise in bipolar transistors
 - Related to the quality/purity of the materials and the processing

Noise in JFET Transistors

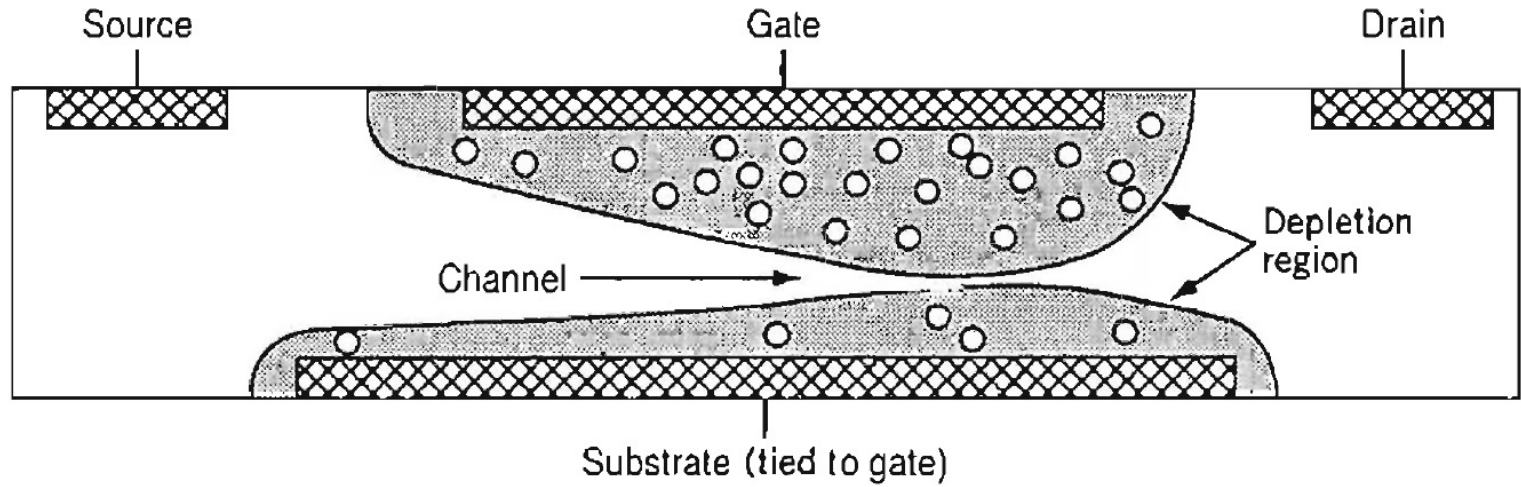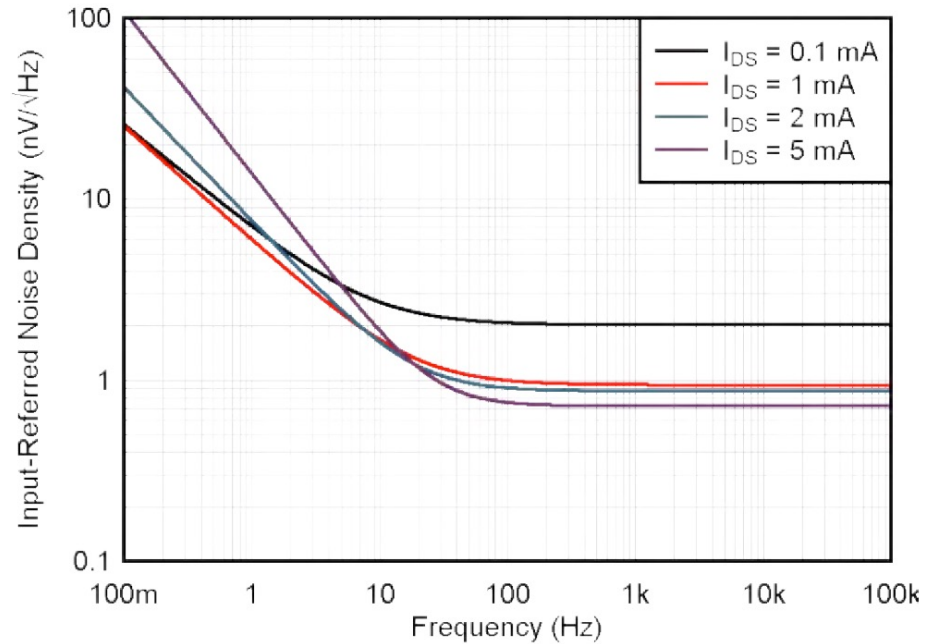


- The voltage noise (V_n) is proportional to the transconductance of the JFET
 - The noise resistance is $R_{noise} \approx \frac{0.67}{g_m}$ Higher g_m implies lower V_n
 - There is a significant 1/f noise corner
- The current noise (I_n) depends on the gate current
 - Which is a reverse biased diode and can be very small (fA/√Hz)
 - Tend to be white with no 1/f noise

Noise in MOSFET Transistors

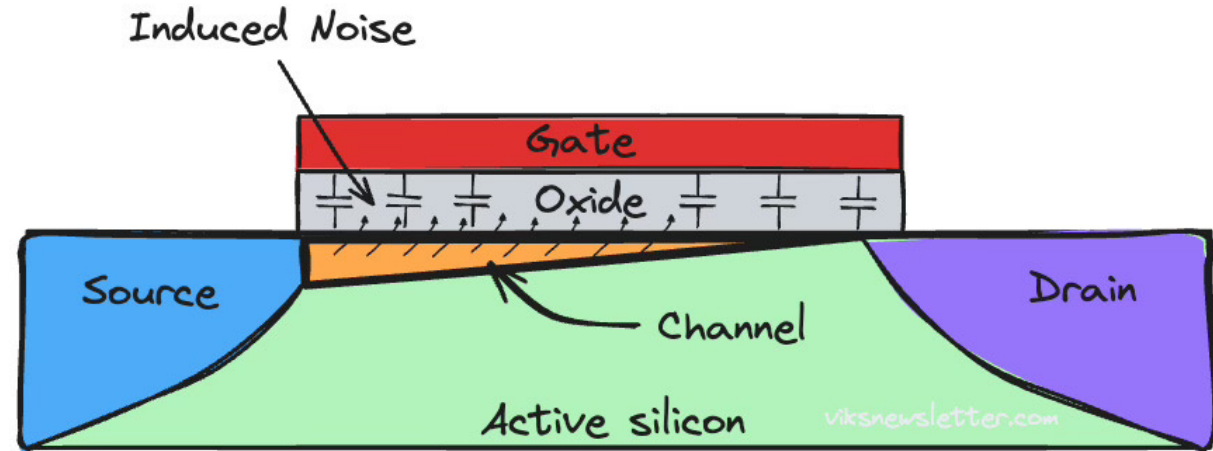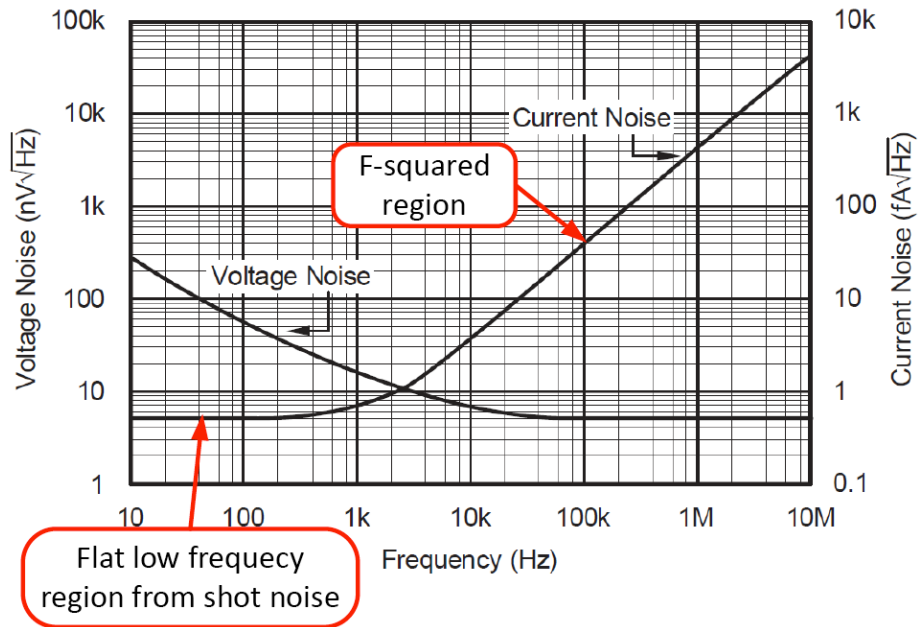


- The voltage noise (V_n) is proportional to the transconductance of the MOSFET
 - The noise resistance is $R_{noise} \approx \frac{0.67}{g_m}$ Higher g_m implies lower V_n
- There is a significant $1/f$ noise corner
 - Due to surface states with the oxide as well as the bulk effects
- There is current noise due to leakage through the gate!
 - And $1/f^2$ noise at high frequencies due induced gate current noise

Noise in Tubes or Valves: Triodes

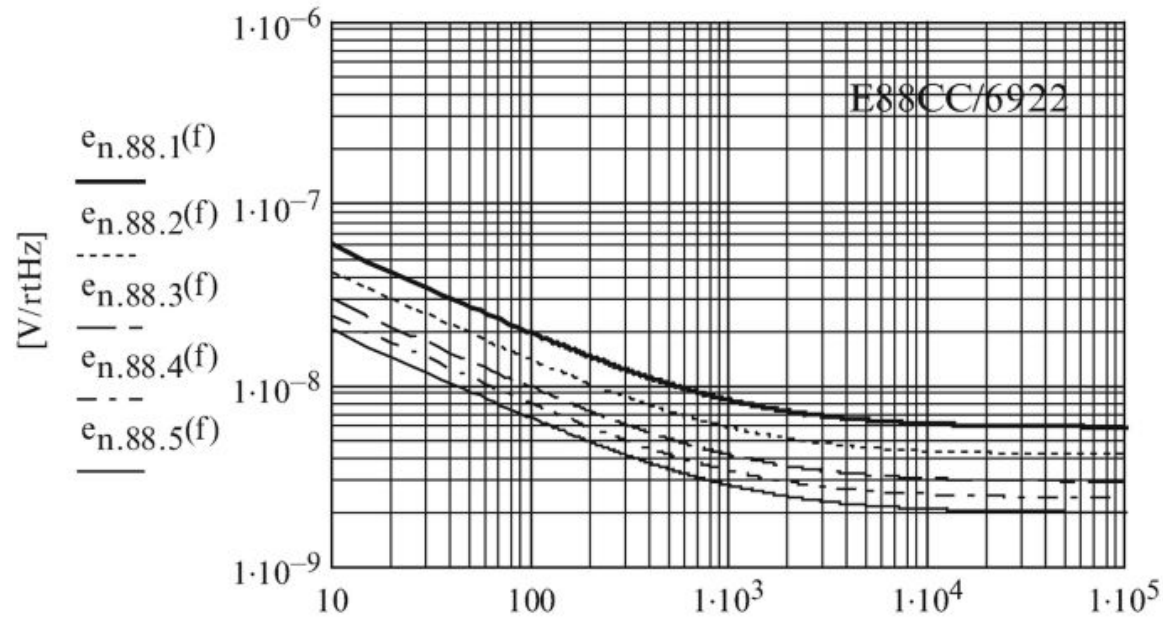

- The voltage noise (V_n) is proportional to the transconductance of the tube/valve
 - The noise resistance is $R_{noise} \approx \frac{3.06}{gm}$ Higher gm implies lower V_n
- There is a significant $1/f$ noise corner
 - Due to surface states within the cathode oxide
- There is current noise due to grid current
 - grid current of the order of 1 – 100 nA
 - corresponding to an input noise current I_n of 18 – 180 $\text{fA}/\sqrt{\text{Hz}}$

Noise in Tubes or Valves: Pentodes



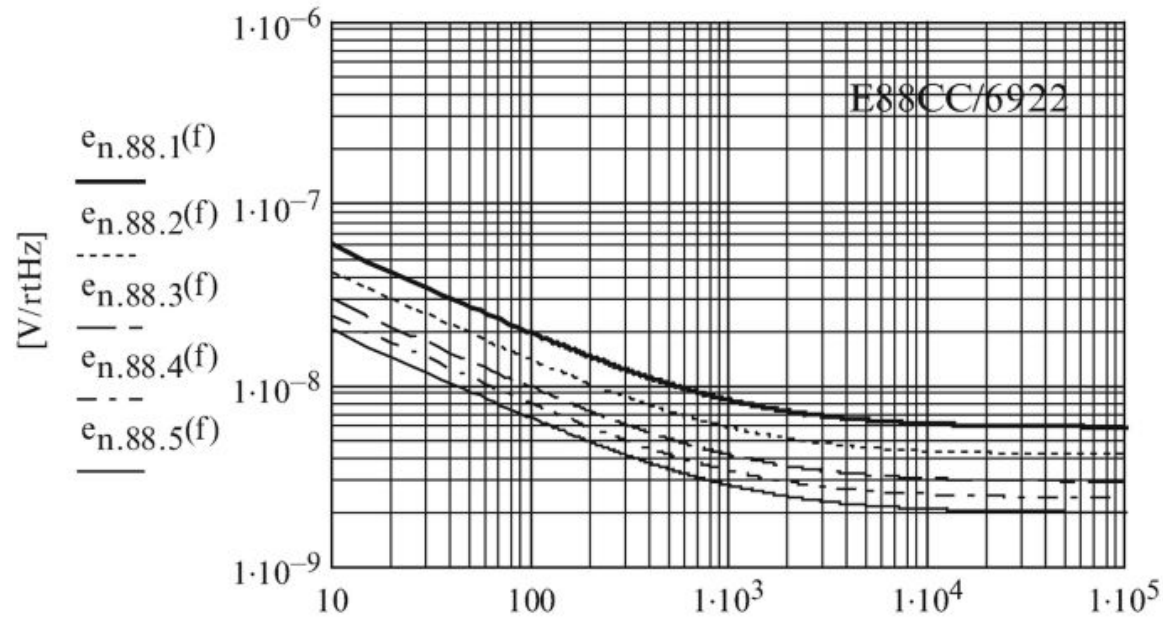


- There is current noise due to the screen grid current I_{sg}
 - Screen grid current I_{sg} is of the order of 3 – 6 mA
 - corresponding to screen noise current I_{nsg} of 31 – 44 $\text{pA}/\sqrt{\text{Hz}}$
 - Which can develop a significant voltage across the $\frac{1}{g_m}$ resistance of the cathode
 - Thus, giving extra “Partition noise”

Independence Of Device Configuration



Common Emitter/Source/Cathode Common Collector/Drain/Anode

Common Base/Gate/Grid

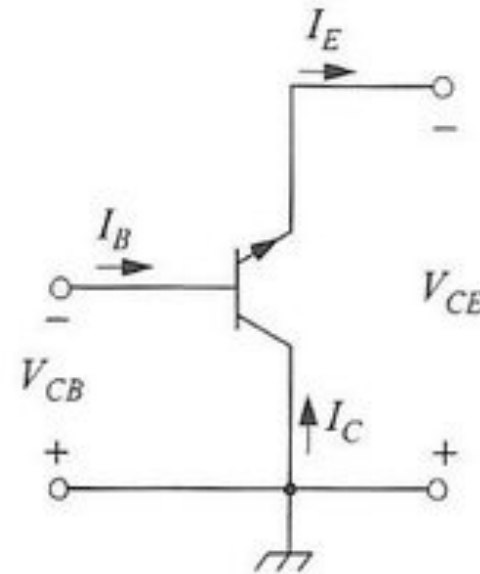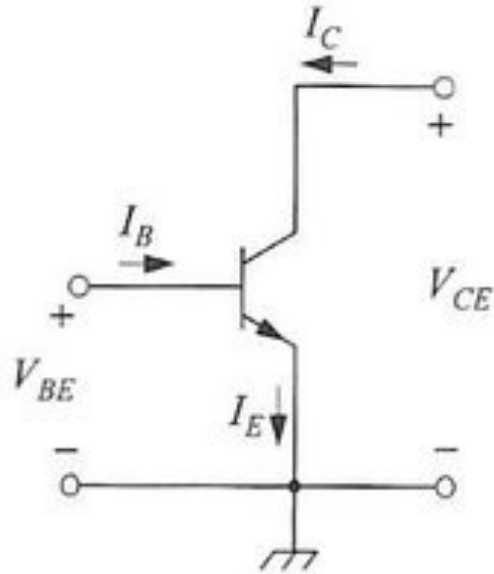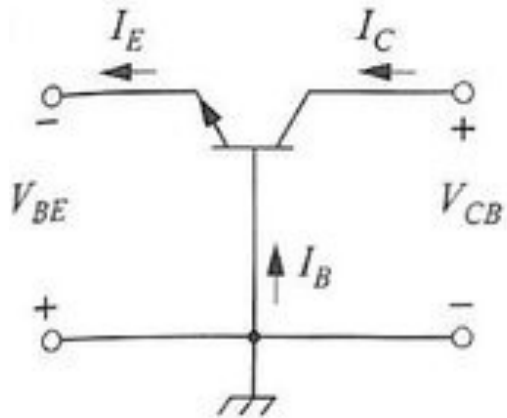


- Irrespective of the devices circuit configuration
 - The voltage noise is still present at the input
 - And the current noise still flows in the input circuit
- The effects of cascading may change
 - For example, the common collector will not be so good for voltage noise when cascaded
 - For current noise however...

Differences in Noise BiFet Versus Mosfet

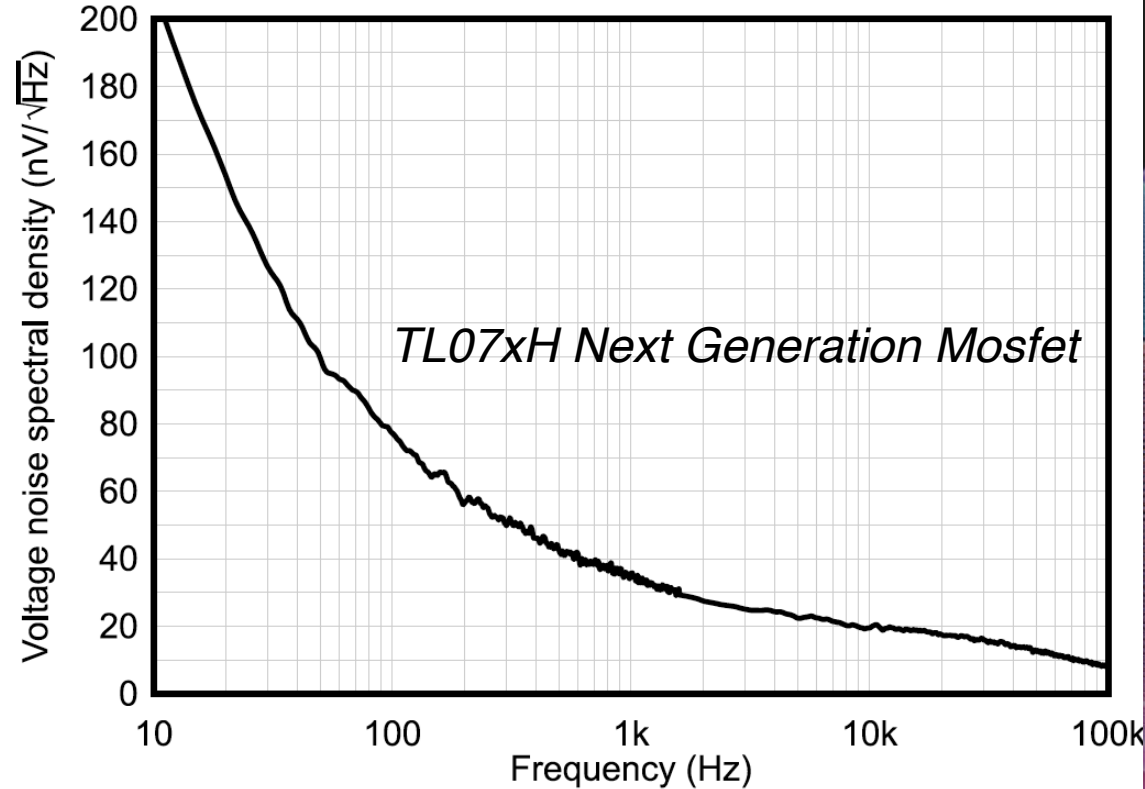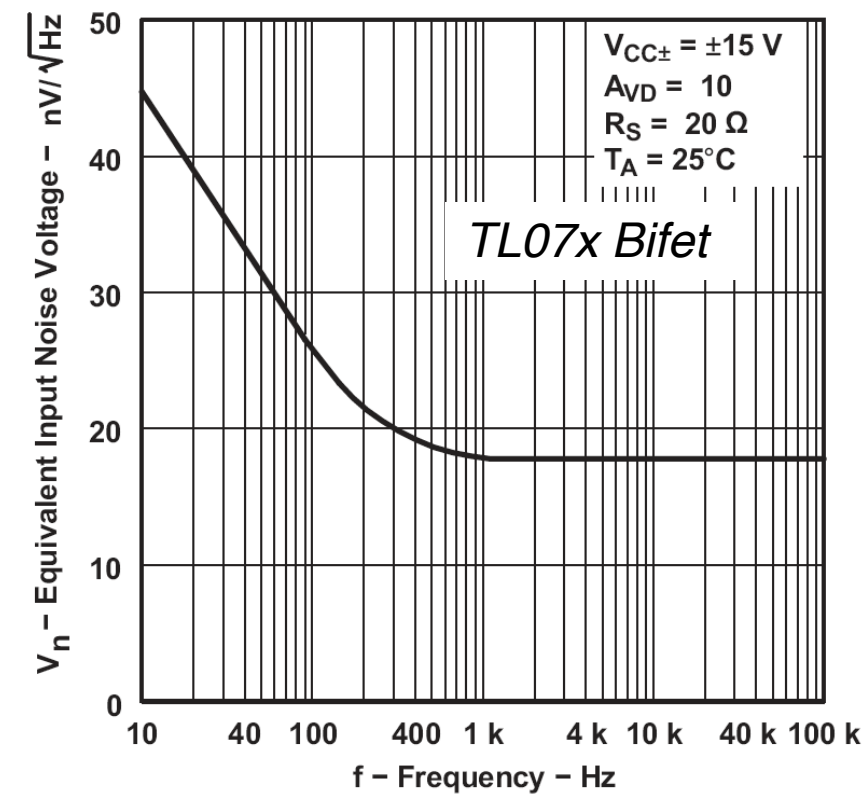


- The BiFet TL07x
 - Junction fet input and bipolar circuitry
 - Has a lower $1/f$ noise corner
- Compared to the all Mosfet TL07xH
 - $1/f$ noise corner is much higher

Two Op Amps... Both Alike in Circuitry

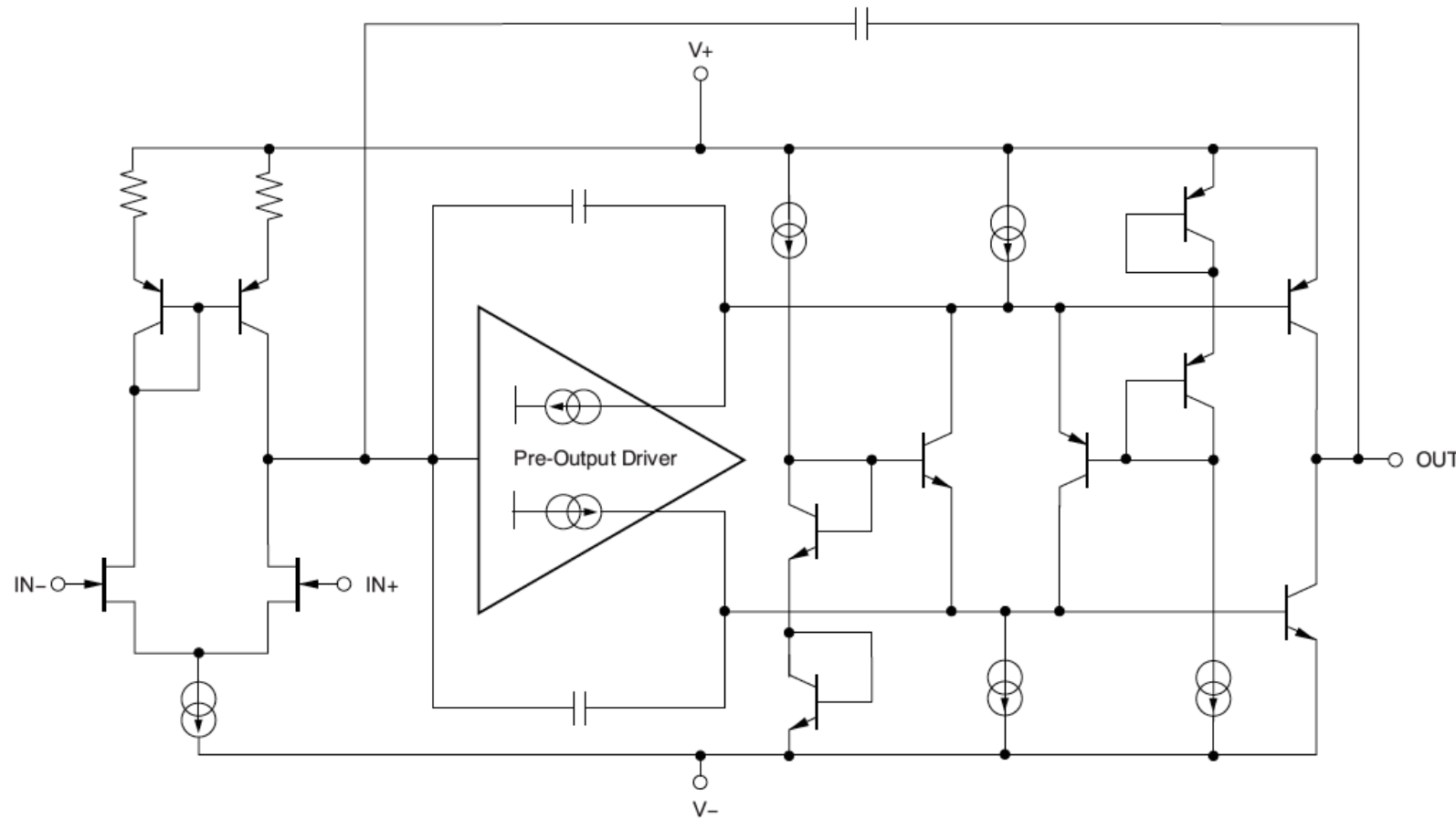


- OPA 1642
 - JFET Input
 - Bipolar, Transimpedance Class AB Output

Two Op Amps... Both Alike in Circuitry

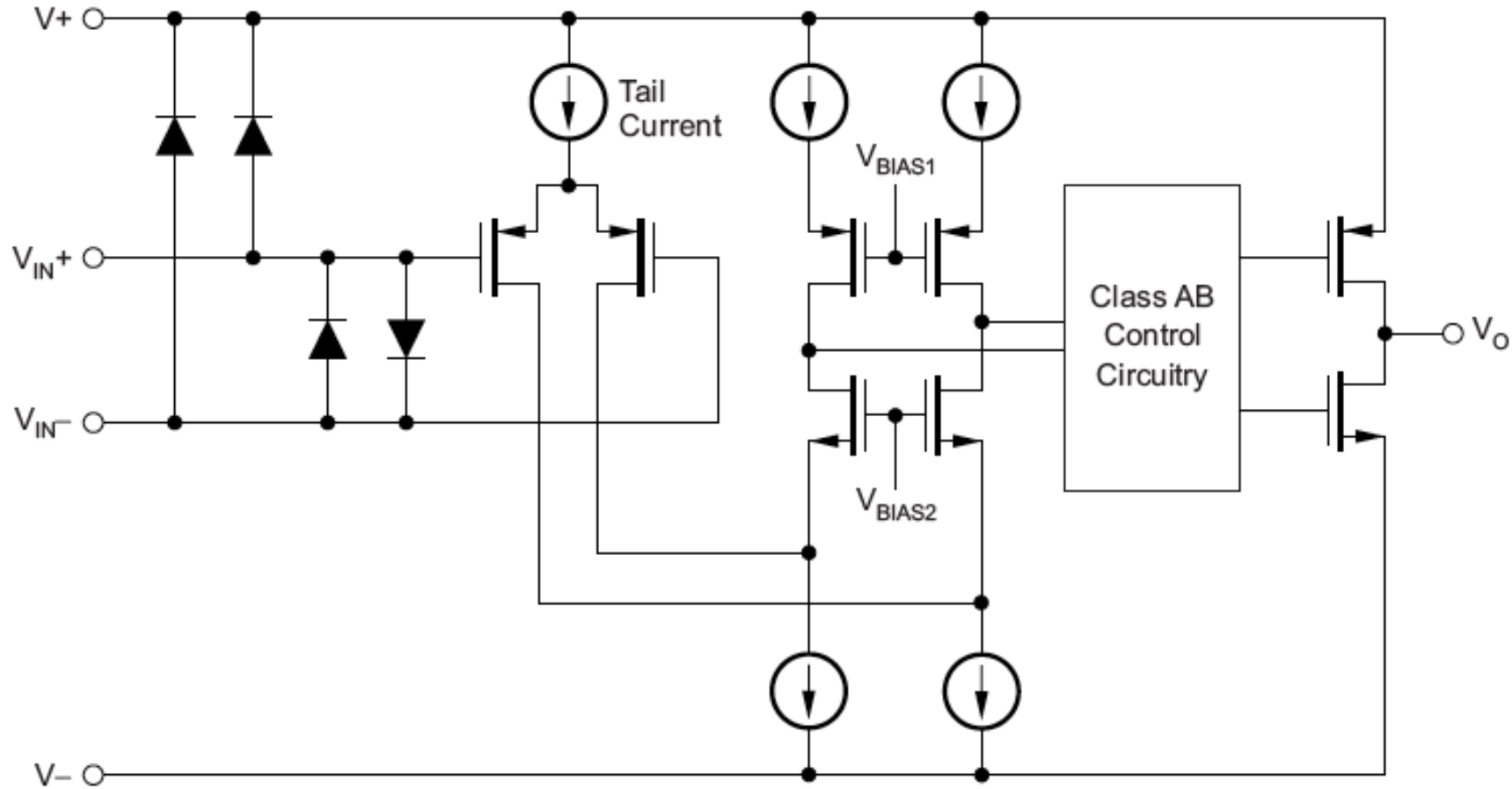

- OPA 1652
 - MOSFET Input
 - MOSFET, Transimpedance Class AB Output


Differences in Noise, Mos Versus Bifet

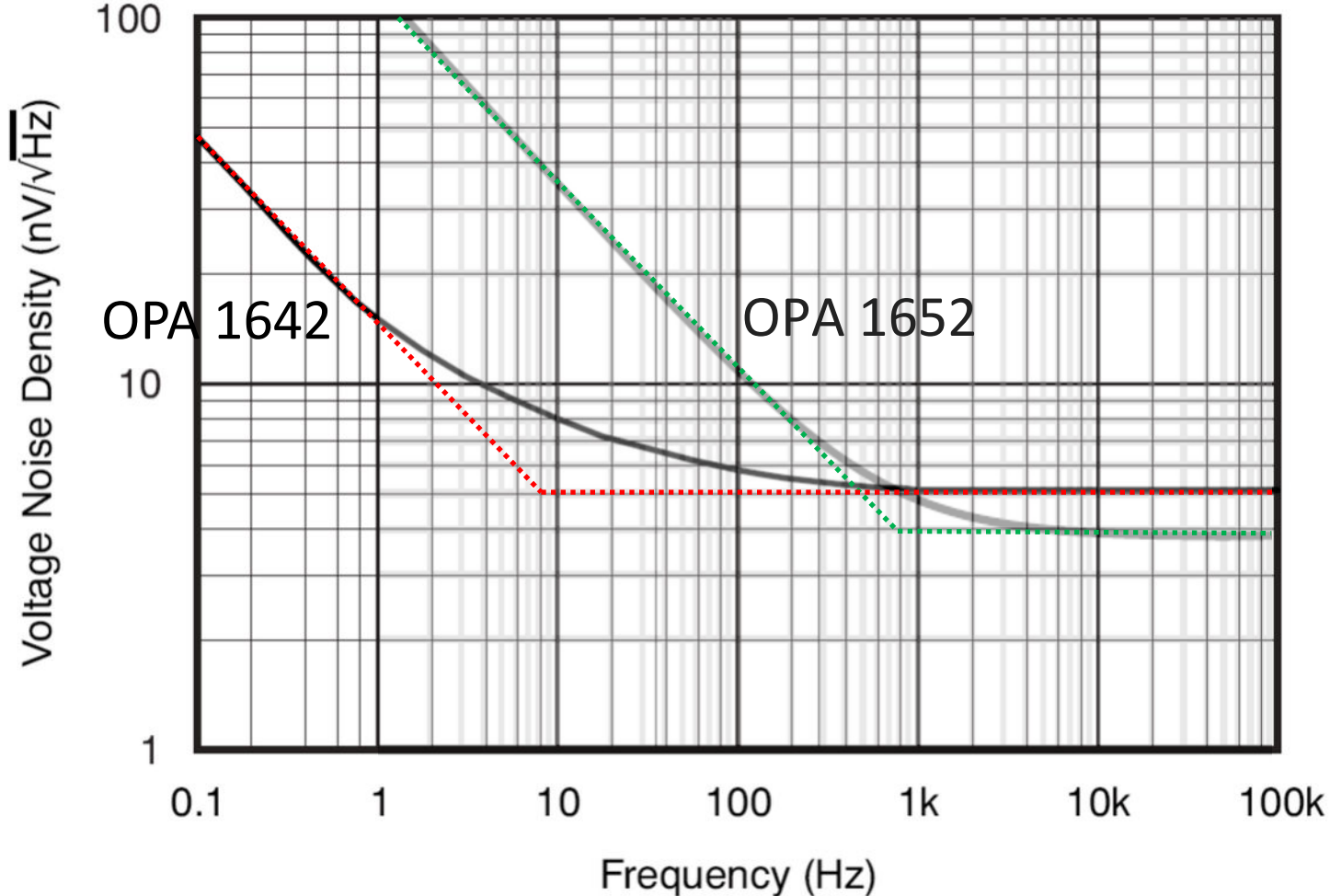

- OPA 1652 has a lower noise floor but a higher corner frequency:
 - Almost a 20 dB difference at low frequencies
 - Matters for Bass controls, RIAA equalization, and Magnetic tape heads


Mimicking Impedance

- Some transducers need to see a particular load
 - Using a resistor is a not the best idea
 - Because it generates extra noise
- It might be better to try and mimic that impedance using feedback
 - For example, using an amplifier with a gain of -10
 - And a resistor that is 11 times larger
 - The effect of the feedback to make it look 11 times smaller
- This will produce less current noise in the transducer

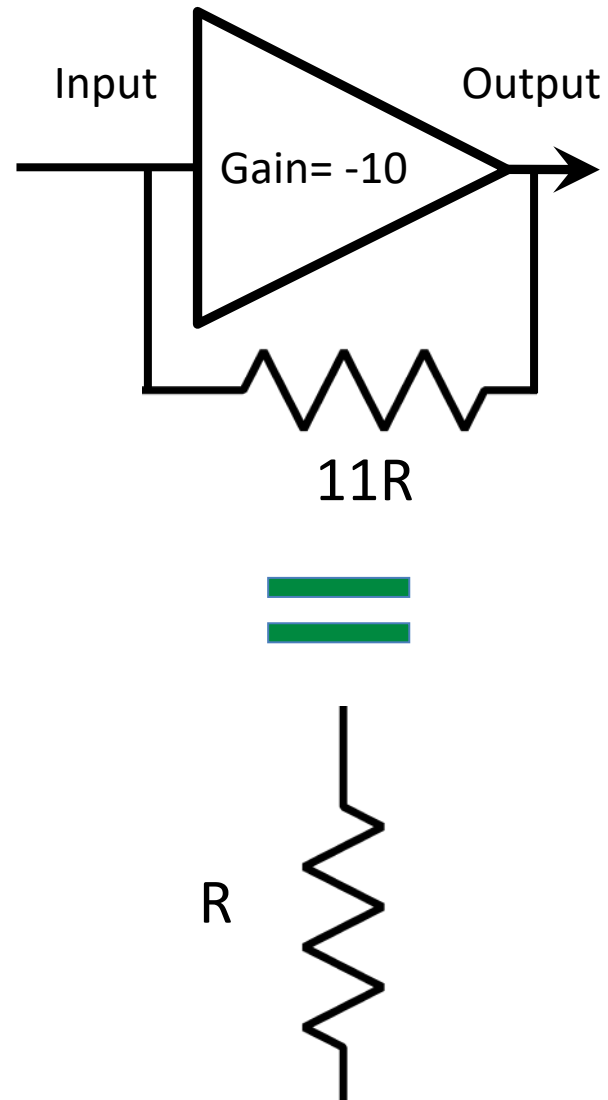


Summing Bus Idea

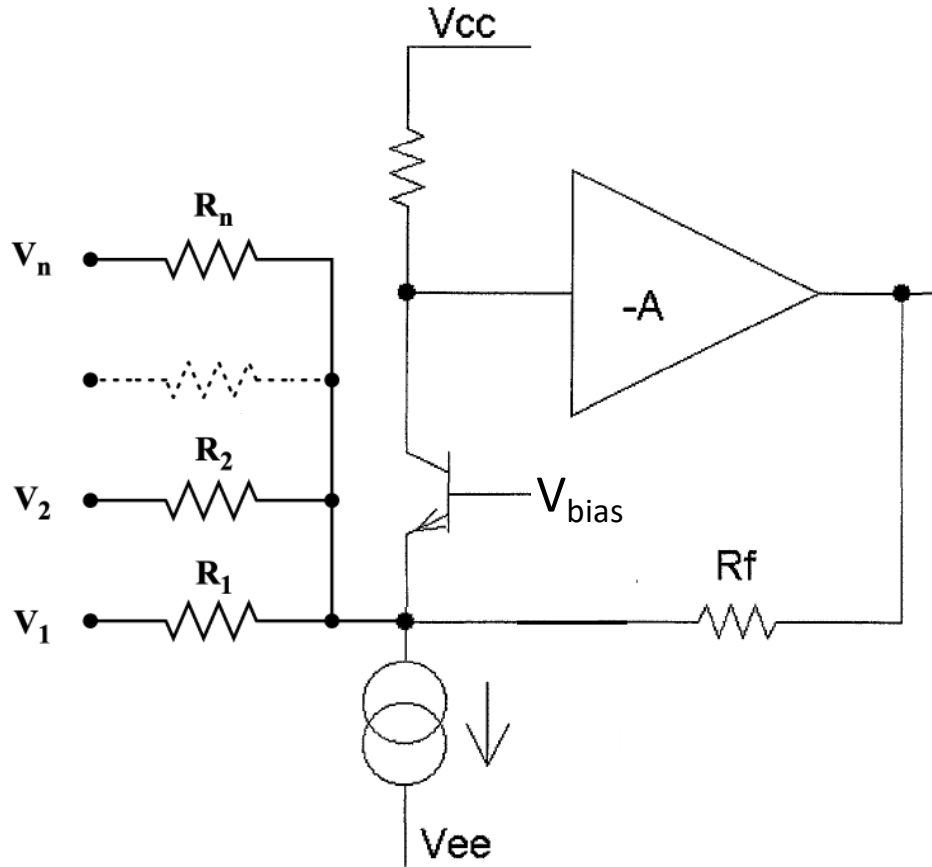- To reduce the signal loss in a summing amplifier
- Feed it into a low impedance point
- Current will then not be attenuated
- By dividing into the other resistors
- Could even use current summing




Digital to Analogue Amp Input cathode

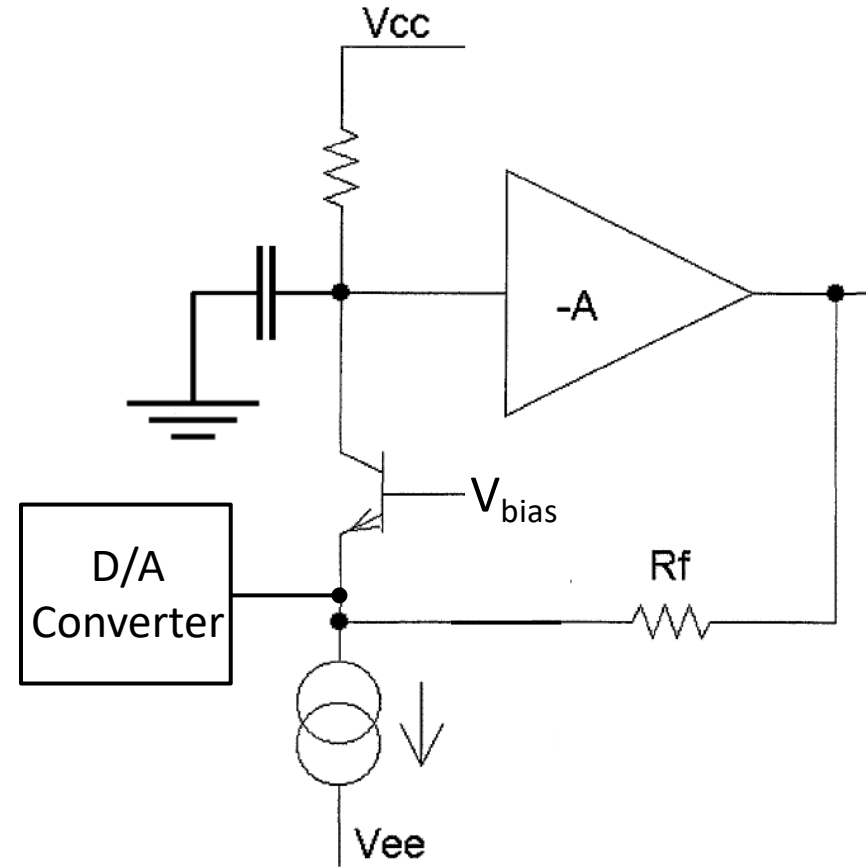- Many Digital to Analogue converters like to see a low impedance
- But they have fast edges etc.
- Using a virtual earth risks dynamic non linearities in the amplifier
- So, using a low impedance point that doesn't require feedback to create it
- Might be a good idea
- One could even slow fast edges down isolated from the D/A circuitry.




Digital to Analogue Amp Cathode Input

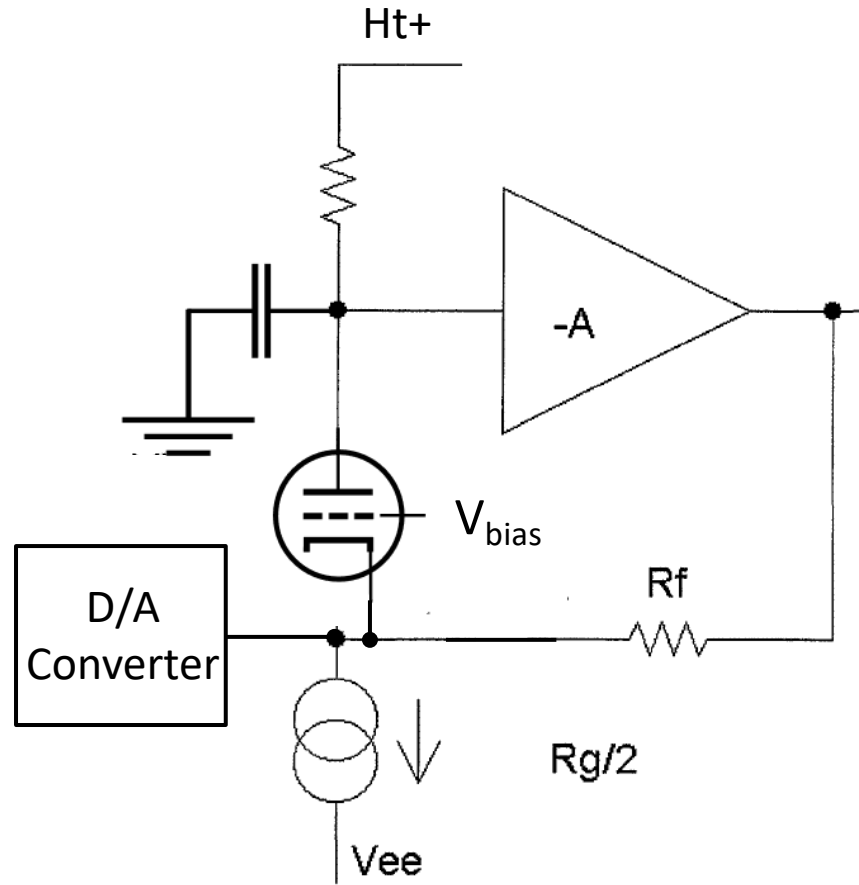
- Many Digital to Analogue converters like to see a low impedance
- But they have fast edges etc.
- Using a virtual earth risks dynamic non linearities in the amplifier
- So, using a low impedance point that doesn't require feedback to create it might be better
- One could even slow fast edges down isolated from the D/A circuitry
- Or use a tube/valve



Summary

- Examined and quantified different sources of noise
 - Developed a universal noise analysis approach using current and voltage noise concepts
- Used it in an example with a resistive transducer
 - And shown the “optimum noise resistance” only applies to resistive sources
 - And shown how reactive transducers need low current and voltage noise and do not have an optimum
- Shown that:
 - V_n is a function of $1/g_m$ irrespective of the device
 - I_n is a function of the devices input current including partition noise
- For low noise:
 - Avoid series resistors
 - And maximise parallel ones
 - Make sure feedback resistors are small enough not to contribute
- Consider circuit remedies to mimic desired load impedances

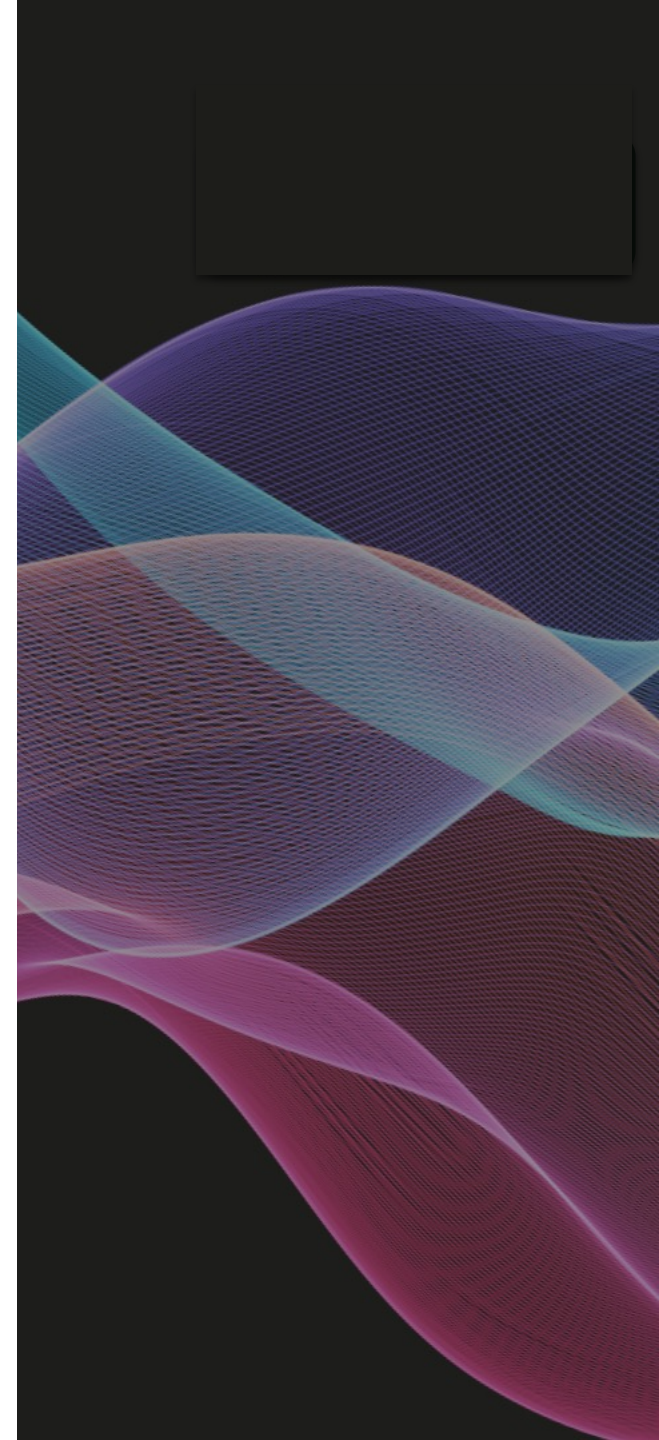

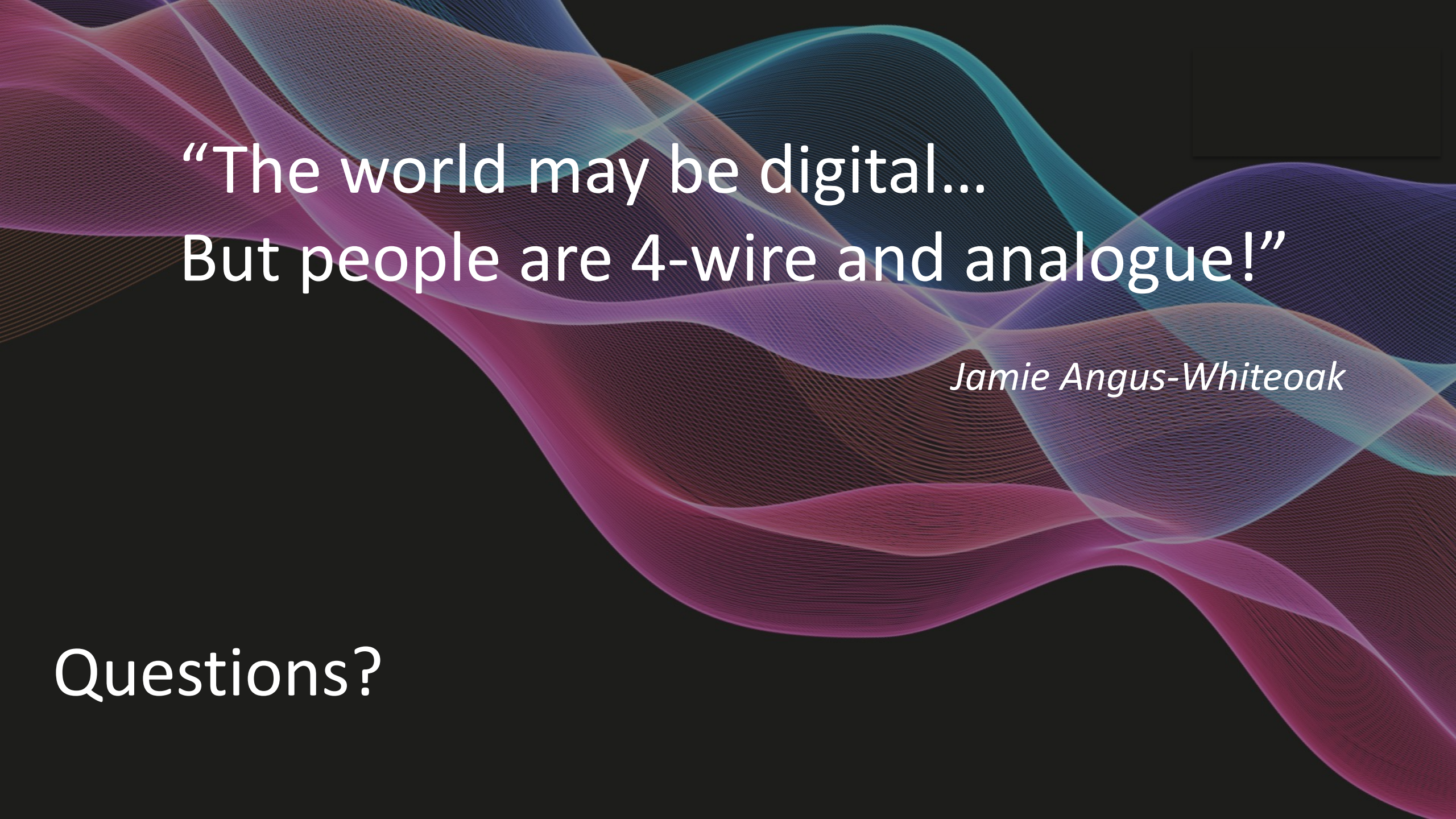

“The world may be digital...
But people are 4-wire and analogue!”

Jamie Angus-Whiteoak

Questions?